

EXPERIMENT No. 01: Write Verilog Code for the following circuits and their Test Bench for verification, observe the waveform and synthesize the code with technological library with given constraints*. Do the initial timing verification with gate level simulation.

i) An inverter

1.1 Objective	1.6 Observation
1.2 Apparatus Required	1.7 Results
1.3 Pre-Requisite	1.8 Discussions
1.4 Introduction	1.9 Pre-Requisite Question
1.5 Procedure	1.10 Post-Requisite

1.1 Objectives:

To write a Verilog and test bench code for an inverter gate and verify the output waveform.

1.2 Apparatus Required:

Cadence Tools.

1.3 Pre-Requisite:

Basic knowledge of verilog coding, CMOS (Complementary Metal Oxide Semiconductor), MOSFET.

1.4 Introduction:

It consists of PMOS and NMOS FET. The input A serves as the gate voltage for both transistors. The NMOS transistor has an input from Vss (ground) and PMOS transistor has an input from Vdd. The terminal Y is output. When a high voltage ($\sim V_{dd}$) is given at input terminal (A) of the inverter, the PMOS becomes open circuit and NMOS switched OFF so the output will be pulled down to Vss.

When a low-level voltage ($< V_{dd}$, $\sim 0V$) applied to the inverter, the NMOS switched OFF and PMOS switched ON. So the output becomes Vdd or the circuit is pulled up to Vdd.


1.5 Procedure:

1. Login to **redhat** operating system with the respective login name and password provided in the lab.
2. Right click on the screen and select **Open Terminal** to open the command prompt.
3. To enter into csh shell type **csh** in the command line.

4. To source the cadence tools type **source /cshrc/cad** in the command line.

STEPS TO COMPLETE AND SIMULATE THE VERILOG CODES

5. The Verilog code and test bench code should be written inside the respected directory



```


Applications Places System
root@vlsi185:~/Desktop
File Edit View Search Terminal Help
[root@vlsi185 Desktop]# csh
[root@vlsi185 ~/Desktop]# source /cad/cshrc

Welcome to Cadence Tools Suite

[root@vlsi185 ~/Desktop]# mkdir inverter
[root@vlsi185 ~/Desktop]# cd inverter
[root@vlsi185 inverter]# gedit inverter.v

```

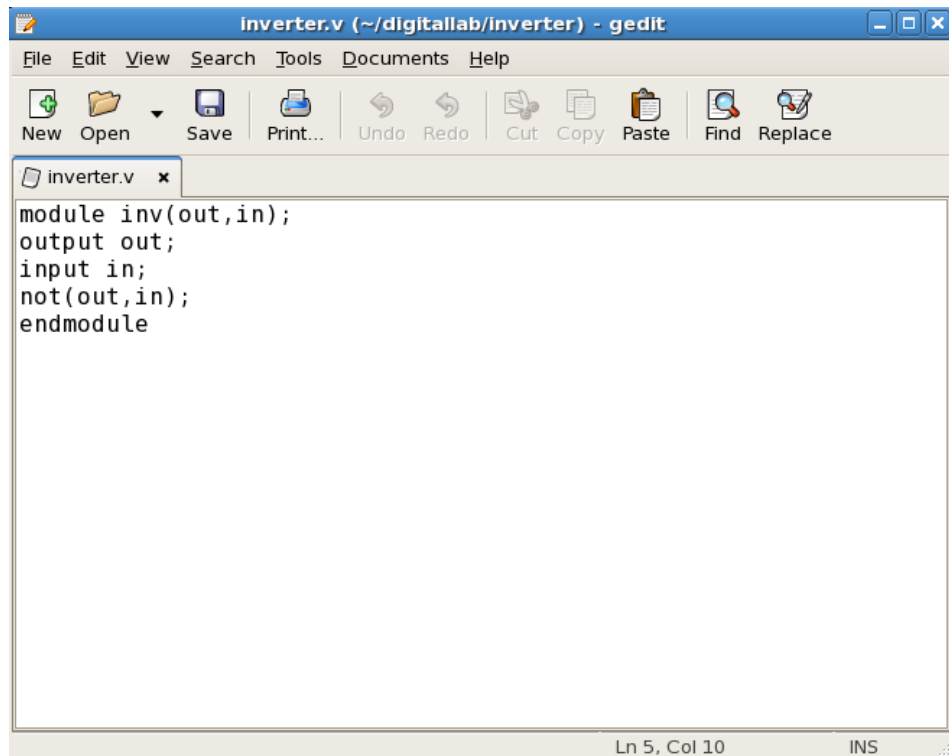6. To write the Verilog code open the editor by typing **gedit<filename.v>** Eg:**gedit inverter.v.**
7. To write the test_bench code open the editor by typing **gedit<filename_test.v>** Eg:**gedit. inverter_test.v.**
8. To compile the verilog program **type ncvlog –mess <filename.v>**, check for errors.
9. To compile the test bench program **type ncvlog –mess <filename_test.v>**, check for errors.



The screenshot shows a gedit window titled "inverter.v (~/.digitallab/inverter) - gedit". The window contains the following Verilog code:

```
module inv(out,in);  
output out;  
input in;  
not(out,in);  
endmodule
```

The status bar at the bottom right indicates "Ln 5, Col 10" and "INS".



The screenshot shows a terminal window titled "root@vlsi-82:~". The terminal displays the following commands and output:


```
[root@vlsi-82 ~]# csh  
[root@vlsi-82 ~]# source cshrc  
Welcome To Cadence Tools Suite  
[root@vlsi-82 ~]# cd digitallab  
[root@vlsi-82 ~/.digitallab]# cd inverter  
[root@vlsi-82 inverter]# gedit inverter.v  
[root@vlsi-82 inverter]# ncvtlog -mess inverter.v  
ncvtlog: 09.20-s055: (c) Copyright 1995-2012 Cadence Design Systems, Inc.  
file: inverter.v  
module worklib.inv  
errors: 0, warnings: 0  
[root@vlsi-82 inverter]# gedit inverter_test.v  
[root@vlsi-82 inverter]# ncvtlog -mess inverter_test.v  
ncvtlog: 09.20-s055: (c) Copyright 1995-2012 Cadence Design Systems, Inc.  
file: inverter_test.v  
module worklib.inverter_test  
errors: 0, warnings: 0  
[root@vlsi-82 inverter]#
```


10. To verify and run the verilog code in the cadence tool type **nclaunch -new** in terminal window




```
root@vlsi-82:~  
File Edit View Terminal Tabs Help  
[root@vlsi-82 ~]# csh  
[root@vlsi-82 ~]# source cshrc  
Welcome To Cadence Tools Suite  
[root@vlsi-82 ~]# cd digitallab  
[root@vlsi-82 ~/digitallab]# cd inverter  
[root@vlsi-82 inverter]# gedit inverter.v  
[root@vlsi-82 inverter]# ncvtlog -mess inverter.v  
ncvtlog: 09.20-s055: (c) Copyright 1995-2012 Cadence Design Systems, Inc.  
file: inverter.v  
    module worklib.invt  
        errors: 0, warnings: 0  
[root@vlsi-82 inverter]# gedit inverter_test.v  
[root@vlsi-82 inverter]# ncvtlog -mess inverter_test.v  
ncvtlog: 09.20-s055: (c) Copyright 1995-2012 Cadence Design Systems, Inc.  
file: inverter_test.v  
    module worklib.invt_test  
        errors: 0, warnings: 0  
[root@vlsi-82 inverter]#
```

11. Select Single Step (IRUN only)

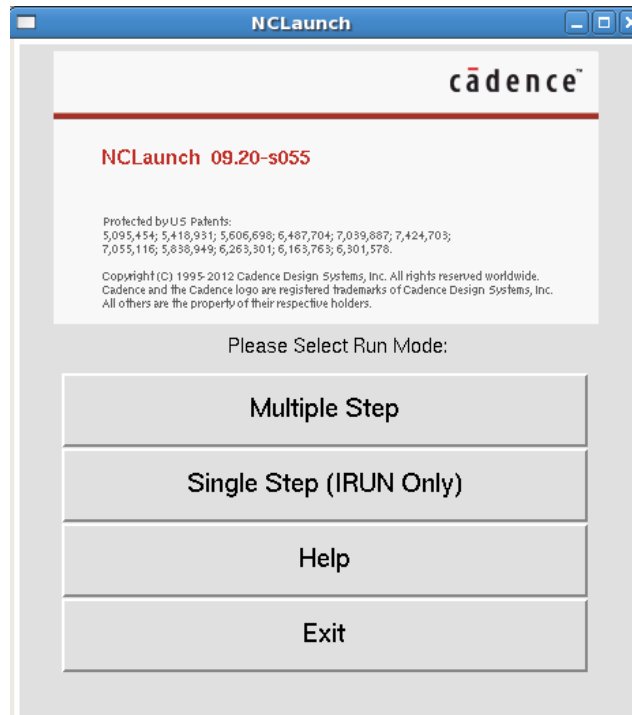

 


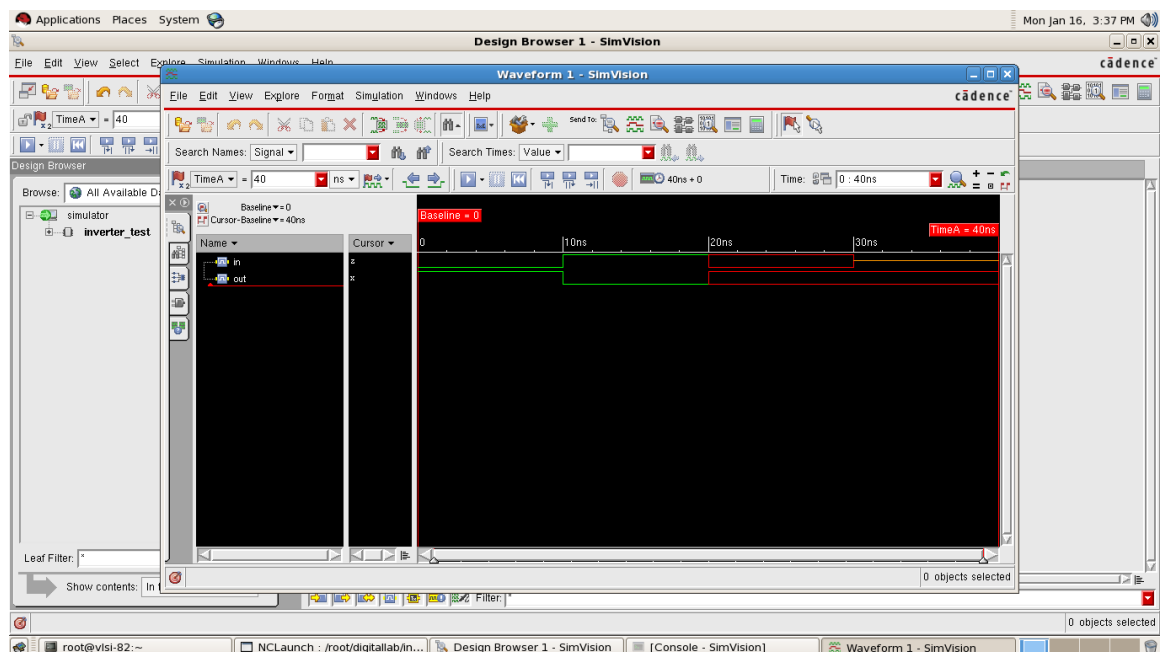12. Now the tool will verify the codes one by one and open a simulation window if there is no error.
13. Double click on the files both test and code files to check for errors.
14. Double click on the launch IRUN with current selection.
15. A new window will appear and in that select in and out right click on it and select the option **send to waveform**.
16. Verify the output.



17. To synthesize the verilog code type **rc -gui** in terminal window.
18. Once enter into gui window type the following commands.

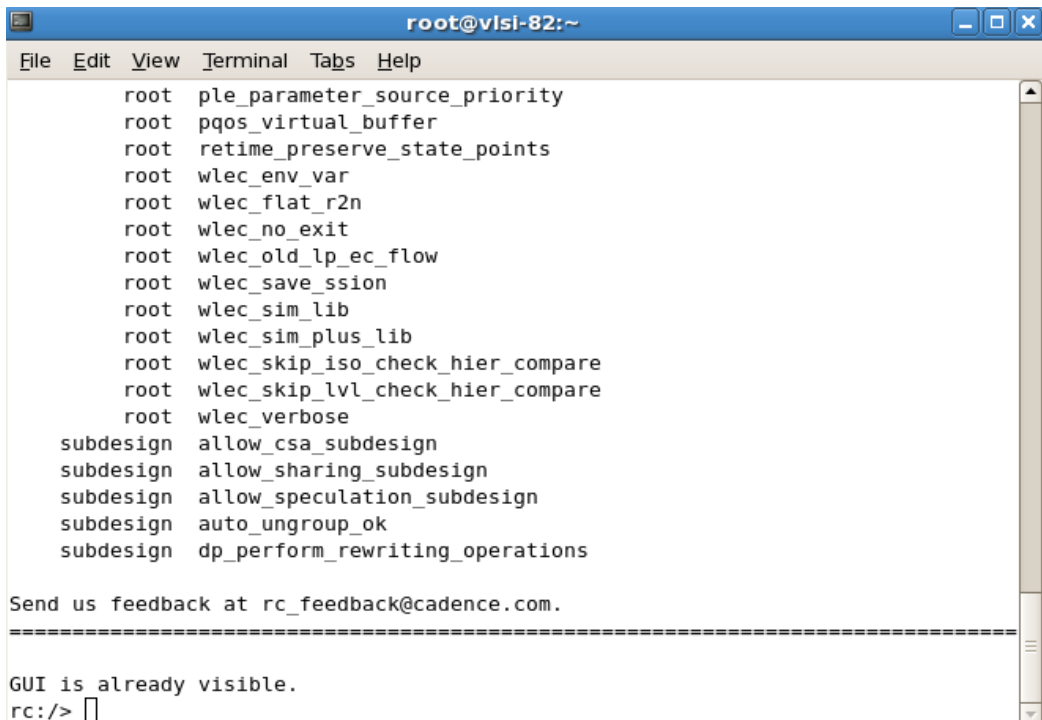19. set_attr lib_search_path <copy and paste the library folder path>
20. set_attr library <copy and paste the slow.lib file path inside the library folder>
21. set_attr hdl_search_path <copy and paste the verilog folder path>
22. read_hdl <filename.v>
23. elaborate



```

root@vlsi-82:~
File Edit View Terminal Tabs Help


root ple_parameter_source_priority
root pqos_virtual_buffer
root retime_preserve_state_points
root wlec_env_var
root wlec_flat_r2n
root wlec_no_exit
root wlec_old_lp_ec_flow
root wlec_save_ssion
root wlec_sim_lib
root wlec_sim_plus_lib
root wlec_skip_iso_check_hier_compare
root wlec_skip_lvl_check_hier_compare
root wlec_verbose
subdesign allow_csa_subdesign
subdesign allow_sharing_subdesign
subdesign allow_speculation_subdesign
subdesign auto_ungroup_ok
subdesign dp_perform_rewriting_operations

Send us feedback at rc_feedback@cadence.com.

=====

GUI is already visible.
rc:/>

```

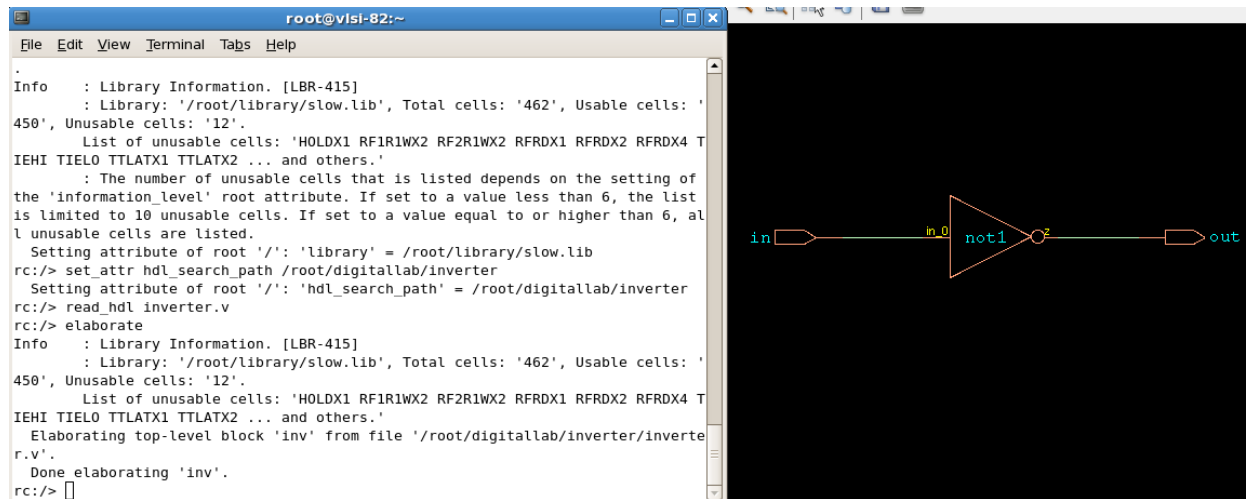


```

root@vlsi-82:~
File Edit View Terminal Tabs Help

.
Info : Library Information. [LBR-415]
      : Library: '/root/library/slow.lib', Total cells: '462', Usable cells: '
450', Unusable cells: '12'.
      : List of unusable cells: 'HOLDX1 RF1R1WX2 RF2R1WX2 RFRDX1 RFRDX2 RFRDX4 T
IEHI TIELO TTLATX1 TTLATX2 ... and others.'
      : The number of unusable cells that is listed depends on the setting of
the 'information_level' root attribute. If set to a value less than 6, the list
is limited to 10 unusable cells. If set to a value equal to or higher than 6, al
l unusable cells are listed.
      : Setting attribute of root '/': 'library' = /root/library/slow.lib
rc:/> set_attr hdl_search_path /root/digitallab/inverter
      : Setting attribute of root '/': 'hdl_search_path' = /root/digitallab/inverte
rc:/> read_hdl inverter.v
rc:/> elaborate
Info : Library Information. [LBR-415]
      : Library: '/root/library/slow.lib', Total cells: '462', Usable cells: '
450', Unusable cells: '12'.
      : List of unusable cells: 'HOLDX1 RF1R1WX2 RF2R1WX2 RFRDX1 RFRDX2 RFRDX4 T
IEHI TIELO TTLATX1 TTLATX2 ... and others.'
      : Elaborating top-level block 'inv' from file '/root/digitallab/inverter/inverte
r.v'.
      : Done elaborating 'inv'.
rc:/>

```

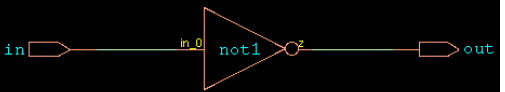

24. Once elaboration done synthesize the code by typing **synthesize** in terminal window.
25. Once synthesize done check for report power, area and gate

```

Applications Places System Mon Jan 16, 3:44 PM
root@visi-82:~
File Edit View Terminal Tabs Help
Done elaborating 'inv'.
rc:/> synthesize
Synthesis succeeded.
rc:/> report power
Warning : Did not find power models for RTL power analysis. [PA-17]
: Design /designs/inv has no power models available.
: The RTL power analysis results are more accurate when detailed power models are used. Use command 'build_rtl_power_models' to build detailed power models.

Generated by:      Encounter(R) RTL Compiler RC10.1.304 - v10.10-s339_1
Generated on:      Jan 16 2017 03:43:57 pm
Module:            inv
Technology library: tsmc18 1.0
Operating conditions: slow (balanced_tree)
Wireload mode:     enclosed
Area mode:         timing library

=====
Leakage   Dynamic   Total
Instance Cells Power(nW) Power(nW) Power(nW)
-----
inv       1       0.114   338.781  338.895

rc:/> report area

Generated by:      Encounter(R) RTL Compiler RC10.1.304 - v10.10-s339_1
Generated on:      Jan 16 2017 03:44:07 pm
Module:            inv
Technology library: tsmc18 1.0
Operating conditions: slow (balanced_tree)
Wireload mode:     enclosed
Area mode:         timing library

=====
Instance Cells Cell Area Net Area Wireload
-----
inv       1       12       0      <none> (D)

(D) = wireload is default in technology library
rc:/>

```

26. Optimize the program using command **synthesize -to_mapped**, and check for report power, area and gate. Compare the report of after and before optimization. Repeat same steps for all the programs.

1.6 Program:

VERILOG CODE:

```

module inv(out,in);

output out;

input in;

not(out,in);

endmodule

```

TEST BENCH CODE:

```

// Declare all inputs as register and output as wire
module inv_test;

wire out;

reg in;

inv a1(out,in); // Instead of a1 can give any names u like other than module name.

initial // All stimulus must be inside initial block, clock must be inside always block.

begin


```

```

#10 in=1'b0;
#10 in=1'b1;
#10 in=1'bx;
#10 in=1'bz;
#10 $finish;
end
endmodule

```

1.7 Results :

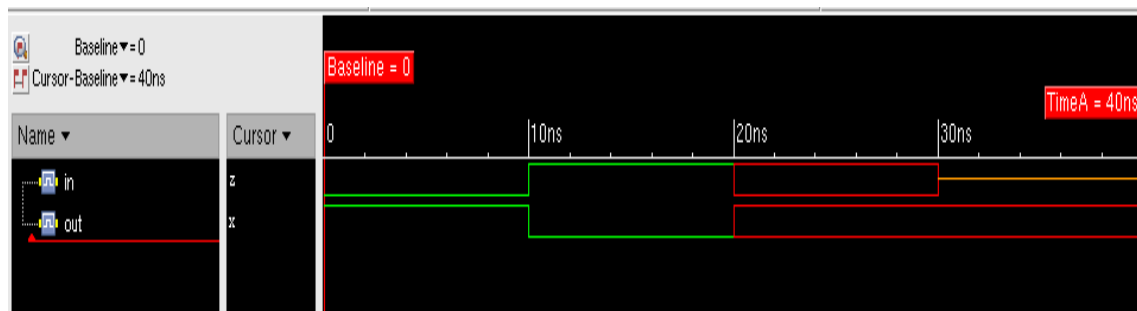

1.8 Discussions:

1.9 Pre – Experimentation Questions:

1. What is MOSFET.
2. Explain the working of MOSFET
3. What is CMOS.
4. Explain the working of CMOS.
5. What is pmos and nmos

1.10 Post – Experimentation Questions:

1. Explain the working of inverter.
2. Explain the characteristics of inverter.
3. Write the truth table of inverter.
4. Write the waveform of inverter.
5. Explain FETs.

ii) A BUFFER

1.1 Objective	1.6 Observation
1.2 Apparatus Required	1.7 Results
1.3 Pre-Requisite	1.8 Discussions
1.4 Introduction	1.9 Pre-Requisite Question
1.5 Procedure	1.10 Post-Requisite

1.1 Objectives:

To write a Verilog and test bench code for buffer and verify the output waveform.

1.2 Apparatus Required:

Cadence Tools.

1.3 Pre-Requisite:

Concept of Buffer.

1.4 Introduction:

A **buffer**, is a basic logic gate that passes its input, unchanged, to its output. Its behavior is the opposite of a NOT gate. The main purpose of a buffer is to regenerate the input, usually using a strong high and a strong low. A buffer has one input and one output; its output always equals its input. Buffers are also used to increase the propagation delay of circuits by driving the large capacitive loads.


1.5 Procedure:

1. Login to **redhat** operating system with the respective login name and password provided in the lab.
2. Right click on the screen and select **Open Terminal** to open the command prompt.
3. To enter into csh shell type **csh** in the command line.
4. To source the cadence tools type **source /cshrc/cad** in the command line.

STEPS TO COMPLETE AND SIMULATE THE VERILOG CODES

5. The Verilog code and test bench code should be written inside the respected directory
6. To write the Verilog code open the editor by typing **gedit<filename.v>** Eg:**gedit buffer.v.**
7. To write the test_bench code open the editor by typing **gedit<filename_test.v>** Eg:**gedit. buffer_test.v.**

 8. To compile the verilog program **type ncvlog –mess <filename.v>**, check for errors.
9. To compile the test bench program **type ncvlog –mess <filename_test.v>**, check for errors.
10. To verify and run the verilog code in the cadence tool type **nclaunch –new** in terminal window.
11. Select **Single Step (IRUN only)**



12. Now the tool will verify the codes one by one and open a simulation window if there is no error.
13. Double click on the files both test and code files to check for errors.
14. Double click on the launch IRUN with current selection.
15. A new window will appear and in that select in and out right click on it and select the option **send to waveform**.
16. Verify the output.
17. To synthesize the verilog code type **rc –gui** in terminal window.
18. Once enter into gui window type the following commands.
19. **set_attr lib_search_path <copy and paste the library folder path>**
20. **set_attr library <copy and paste the slow.lib file path inside the library folder>**
21. **set_attr hdl_search_path <copy and paste the verilog folder path>**

22. read_hdl <filename.v>
23. elaborate
24. Once elaboration done synthesize the code by typing **synthesize** in terminal window.
25. Once synthesize done check for report power, area and gate
26. Optimize the program using command **synthesize –to_mapped**, and check for report power, area and gate. Compare the report of after and before optimization. Repeat same steps for all the programs.

1.6 Program:


VERILOG CODE:

```
module buffer(a,c,y);
input a;
output y;
inout c;
assign c=~a;
assign y=~c;
endmodule
```

TEST BENCH CODE:

```
module buffer_test;
reg a;
wire c;
wire y;
buffer a1(a,c,y);
initial
begin
$monitor ($time,"c=%d,y=%d" c,y);
#10 a=1'b0;
#10 a=1'b1;
#10 a=1'b0;
#10 $finish;
end
endmodule
```

1.7 Results :

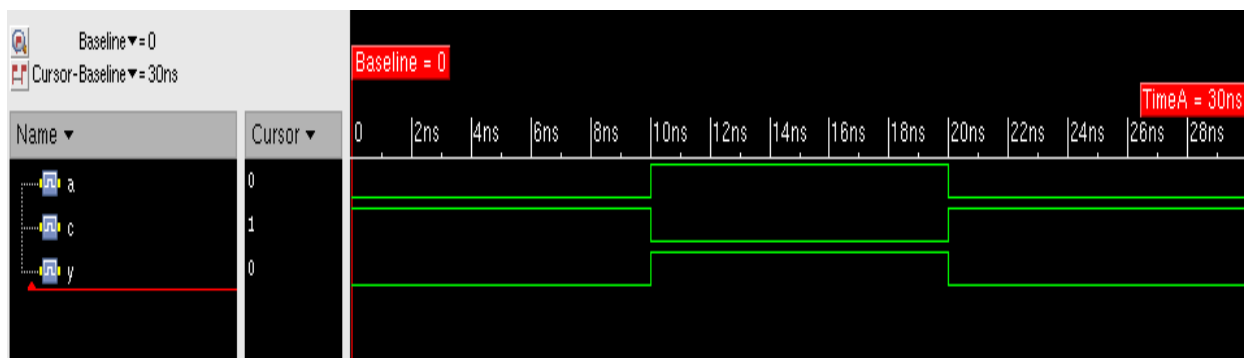

1.8 Discussions:

1.9 Pre – Experimentation Questions:

1. What is buffer.
2. Working of PMOS
3. Explain working of NMOS
4. Explain the working of inverter
5. Write the symbol of inverter

1.10 Post – Experimentation Questions:

1. Explain the working of Buffer.
2. Explain the characteristics of Buffer.
3. Write the symbol of Buffer.
4. Write the waveform for buffer.
5. Explain the working of each stage in Buffer.

iii) Transmission Gate

1.1 Objective	1.6 Observation
1.2 Apparatus Required	1.7 Results
1.3 Pre-Requisite	1.8 Discussions
1.4 Introduction	1.9 Pre-Requisite Question
1.5 Procedure	1.10 Post-Requisite

1.1 Objectives:

To write a Verilog and test bench code for Transmission gate and verify the output waveform.

1.2 Apparatus Required:

Cadence Tools.

1.3 Pre-Requisite:

Knowledge of PMOS, NMOS, CMOS.

1.4 Introduction:

A **transmission gate (TG)** it is analog gate similar to a relay that can conduct in both directions or block by a control signal with almost any voltage potential. It is a CMOS-based switch, in which PMOS passes a strong 1 but poor 0, and NMOS passes strong 0 but poor 1. Both PMOS and NMOS work simultaneously.


1.5 Procedure:

1. Login to **redhat** operating system with the respective login name and password provided in the lab.
2. Right click on the screen and select **Open Terminal** to open the command prompt.
3. To enter into csh shell type **csh** in the command line.
4. To source the cadence tools type **source /cshrc/cad** in the command line.

STEPS TO COMPLETE AND SIMULATE THE VERILOG CODES

5. The Verilog code and test bench code should be written inside the respected directory
6. To write the Verilog code open the editor by typing **gedit<filename.v>** Eg:**gedit transmission.v.**
7. To write the test_bench code open the editor by typing **gedit<filename_test.v>** Eg:**gedit. transmission_test.v.**
8. To compile the verilog program type **ncvlog –mess <filename.v>**, check for errors.

 9. To compile the test bench program type **ncvlog -mess <filename_test.v>**, check for errors.
10. To verify and run the verilog code in the cadence tool type **nclaunch -new** in terminal window.
11. Select **Single Step (IRUN only)**



12. Now the tool will verify the codes one by one and open a simulation window if there is no error.
13. Double click on the files both test and code files to check for errors.
14. Double click on the launch IRUN with current selection.
15. A new window will appear and in that select in and out right click on it and select the option **send to waveform**.
16. Verify the output.
17. To synthesize the verilog code type **rc -gui** in terminal window.
18. Once enter into gui window type the following commands.
19. **set_attr lib_search_path <copy and paste the library folder path>**
20. **set_attr library <copy and paste the slow.lib file path inside the library folder>**
21. **set_attr hdl_search_path <copy and paste the verilog folder path>**

22. read_hdl <filename.v>
23. elaborate
24. Once elaboration done synthesize the code by typing **synthesize** in terminal window.
25. Once synthesize done check for report power, area and gate
26. Optimize the program using command **synthesize –to_mapped**, and check for report power, area and gate. Compare the report of after and before optimization. Repeat same steps for all the programs.

1.6 Program:

VERILOG CODE:

```

module transgate(s,x,y);
input s,x;
output y;
reg y;
always@ (x or s)
begin
if(x==0 && s==1)
y =1'b0;
if(x==1 && s==1)
y =1'b1;
if( s == 0)
y=1'bx;
end
endmodule

```

TEST BENCH CODE:

```

module transgate_test;
reg x,s;
wire y;
transgate a1(s,x,y);
initial
begin


```

```

$monitor($time,"y=%d",y);
x=1'b0;
s=1'b1;
#10 x=1'b1;
s=1'b1;
#10 x=1'b0;
s=1'b0;
#10 x=1'b1;
s=1'b0;
#10 $finish;
end
endmodule

```

1.7 Results :

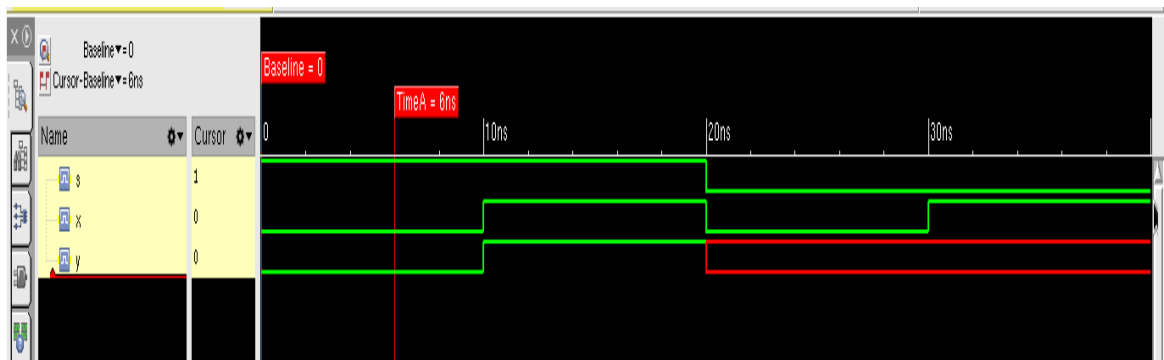

1.8 Discussions:

1.9 Pre – Experimentation Questions:

1. Explain the working of NMOS and PMOS.
2. Discuss the theoretical working.
3. Explain the working of buffer.
4. Draw the circuit for TG.
5. Analyze the theoretical working of TG

1.10 Post – Experimentation Questions:

1. Explain the functioning of TG
2. Discuss TG characteristics.
3. Explain the verilog code written for TG
4. Write the symbol for TG.
5. Explain the waveform of TG.

iv) Basic/Universal Gate

1.1 Objective	1.6 Observation
1.2 Apparatus Required	1.7 Results
1.3 Pre-Requisite	1.8 Discussions
1.4 Introduction	1.9 Pre-Requisite Question
1.5 Procedure	1.10 Post-Requisite

1.1 Objectives:

To write a Verilog and test bench code for Basic/Universal gate and verify the output waveform.

1.2 Apparatus Required:

Cadence Tools.

1.3 Pre-Requisite:

Basic knowledge of digital logic gates and Boolean algebra.

1.4 Introduction:

Digital systems are said to be constructed by using logic **gates**. These **gates** are the AND, OR, NOT, NAND, NOR, EXOR and EXNOR **gates**. NAND gate and NOR gate are universal logic gates because any boolean function can be implemented using one of these gates.


1.5 Procedure:

1. Login to **redhat** operating system with the respective login name and password provided in the lab.
2. Right click on the screen and select **Open Terminal** to open the command prompt.
3. To enter into csh shell type **csh** in the command line.
4. To source the cadence tools type **source /cshrc/cad** in the command line.

STEPS TO COMPLETE AND SIMULATE THE VERILOG CODES

5. The Verilog code and test bench code should be written inside the respected directory
6. To write the Verilog code open the editor by typing **gedit<filename.v>** Eg:**gedit basic.v**.
7. To write the test_bench code open the editor by typing **gedit<filename_test.v>** Eg:**gedit. basic_test.v**.
8. To compile the verilog program type **ncvlog –mess <filename.v>**, check for errors.

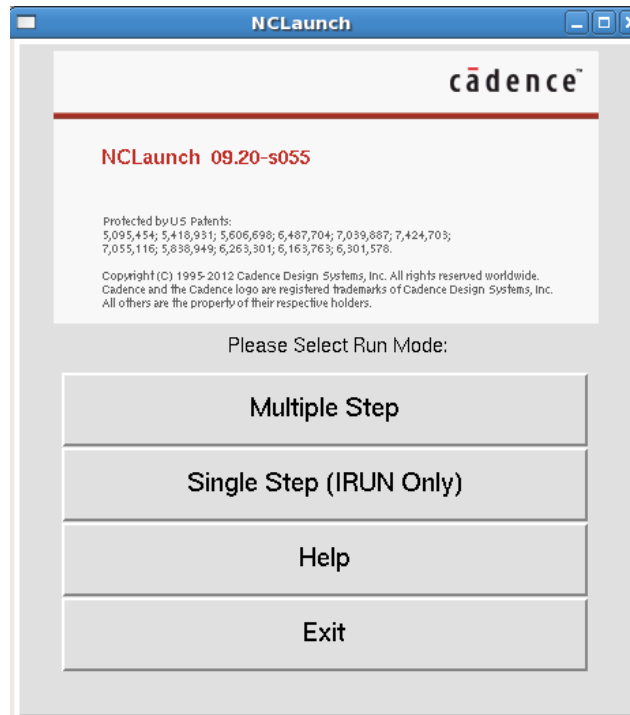9. To compile the test bench program type **ncvlog -mess <filename_test.v>**, check for errors.
10. To verify and run the verilog code in the cadence tool type **nclaunch -new** in terminal window.
11. Select **Single Step (IRUN only)**



12. Now the tool will verify the codes one by one and open a simulation window if there is no error.
13. Double click on the files both test and code files to check for errors.
14. Double click on the launch IRUN with current selection.
15. A new window will appear and in that select in and out right click on it and select the option **send to waveform**.
16. Verify the output.
17. To synthesize the verilog code type **rc -gui** in terminal window.
18. Once enter into gui window type the following commands.
19. **set_attr lib_search_path <copy and paste the library folder path>**
20. **set_attr library <copy and paste the slow.lib file path inside the library folder>**
21. **set_attr hdl_search_path <copy and paste the verilog folder path>**

22. read_hdl <filename.v>
23. elaborate
24. Once elaboration done synthesize the code by typing **synthesize** in terminal window.
25. Once synthesize done check for report power, area and gate
26. Optimize the program using command **synthesize –to_mapped**, and check for report power, area and gate. Compare the report of after and before optimization. Repeat same steps for all the programs.

1.6 Program:

VERILOG CODE:

```

module allgate (a,b,y);
input a,b;
output [1:8]y;
assign y[1]=a+b;
assign y[2]=a|b;
assign y[3]=~a;
assign y[4]=~(a+b);
assign y[5]=~(a|b);
assign y[6]=a^b;
assign y[7]=a&b;
assign y[8]=~(a&b);
endmodule

```

TEST BENCH CODE:

```

module tb_allgate;
reg a,b;
wire [1:8]y;
allgate a1(a,b,y);
initial
begin
a=1'b0;
forever #100 a=~a;
end


```

```

initial
begin
b=1'b0;
forever #200 b=~b;
end
endmodule

```

1.7 Results :

 

1.8 Discussions:

1.9 Pre – Experimentation Questions:

1. Define logic gates.
2. Explain the Boolean algebra.
3. Write the truth table for AND gate.
4. Write the truth table for OR gate.
5. Write the truth table for NOR and NAND gate.

1.10 Post – Experimentation Questions:

1. Explain working of basic gates and universal gates.
2. Write the symbol of basic gates.
3. List the universal gates and draw the symbols
4. Explain the verilog code for the same.
5. What is wire in verilog.

v) Flip Flops

1.1 Objective	1.6 Observation
1.2 Apparatus Required	1.7 Results
1.3 Pre-Requisite	1.8 Discussions
1.4 Introduction	1.9 Pre-Requisite Question
1.5 Procedure	1.10 Post-Requisite

1.1 Objectives:

To write a Verilog and test bench code for RS, D, JK, MS,T Flip Flops and verify the output waveform.

1.2 Apparatus Required:

Cadence Tools.

1.3 Pre-Requisite:

Basic knowledge of Latch, memory.

1.4 Introduction:

A flip flop is an electronic circuit with two stable states that can be used to store binary data. The stored data can be changed by applying varying inputs. Flip-flops and latches are fundamental building blocks of digital electronics systems used in computers, communications, and many other types of systems. Flip-flops and latches are used as data storage elements. It is the basic storage element in sequential logic.


1.5 Procedure:

1. Login to **redhat** operating system with the respective login name and password provided in the lab.
2. Right click on the screen and select **Open Terminal** to open the command prompt.
3. To enter into csh shell type **csh** in the command line.
4. To source the cadence tools type **source /cshrc/cad** in the command line.

STEPS TO COMPLETE AND SIMULATE THE VERILOG CODES

5. The Verilog code and test bench code should be written inside the respected directory
6. To write the Verilog code open the editor by typing **gedit<filename.v>** Eg:**gedit flop.v.**

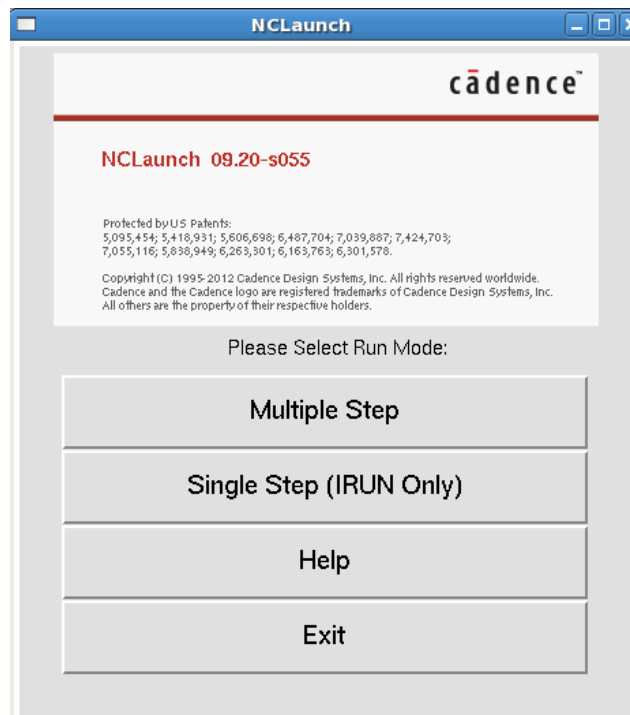7. To write the test_bench code open the editor by typing **gedit<filename_test.v>**
Eg:**gedit. flop_test.v.**
8. To compile the verilog program **type ncvlog –mess <filename.v>**, check for errors.
9. To compile the test bench program **type ncvlog –mess <filename_test.v>**, check for errors.
10. To verify and run the verilog code in the cadence tool type **nclaunch –new** in terminal window.
11. Select **Single Step (IRUN only)**



12. Now the tool will verify the codes one by one and open a simulation window if there is no error.
13. Double click on the files both test and code files to check for errors.
14. Double click on the launch IRUN with current selection.
15. A new window will appear and in that select in and out right click on it and select the option **send to waveform.**
16. Verify the output.
17. To synthesize the verilog code type **rc –gui** in terminal window.
18. Once enter into gui window type the following commands.
19. **set_attr lib_search_path <copy and paste the library folder path>**

20. **set_attr library** <copy and paste the slow.lib file path inside the library folder>
21. **set_attr hdl_search_path** <copy and paste the verilog folder path>
22. **read_hdl** <filename.v>
23. **elaborate**
24. Once elaboration done synthesize the code by typing **synthesize** in terminal window.
25. Once synthesize done check for report power, area and gate
26. Optimize the program using command **synthesize –to_mapped**, and check for report power, area and gate. Compare the report of after and before optimization. Repeat same steps for all the programs.

1.6 Program:

RS FLIPFLOP

VERILOG CODE:

```

module srff(q,qb,s,r,clk,rst);
output q,qb;
input clk,s,r,rst;
reg tq;
always@ (posedge clk or posedge rst)
begin
if(rst==1)
tq<=1'b0;
else
begin
if (s==1'b0 && r==1'b0)
tq<=tq;
else if(s==1'0 && r==1'b1)
tq<=1'b0;
else if(s==1'b1 && r==1'b0)
tq<=1'b1;
else if(s==1'b1 && r==1'b1)
tq<=1'bx;
end
end

```



```
end
assign q=tq;
assign qb=~tq;
endmodule
```


TESTBENCH CODE:

```
module srff_test;
reg clk,s,r,rst;
wire q,qb;
srff sr1(q,qb,s,r,clk,rst);
initial
clk=1'b0;
always
#10 clk=~clk;
initial
begin
rst=1'b1;
s=1'b1;
r=1'b0;
#10 s=1'b0;
#10 r=1'b1;
#10 rst=1'b0;
#10 s=1'b1;
r=1'b0;
#10 s=1'b0;
r=1'b0;
#10 s=1'b0;

r=1'b1;
#10 rst=1'b1;
#10 s=1'b1;
r=1'b0;
end
initial
```

```
#500 $finish;
endmodule
```

1.7 Results :

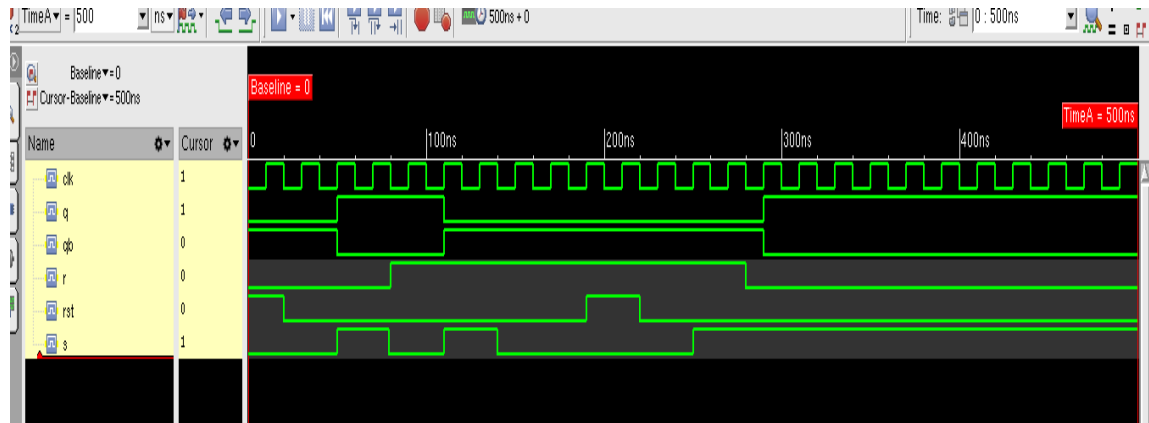

D FLIPFLOP

VERILOG CODE:


```
module dff(d,q,qd,clk);
input d,clk;
output q,qd;
reg q,qd;
initial
begin
q=0;
end
always@(posedge clk)
begin
if(d==0)
q=0;
else
q=1;
qd=~q;
end
endmodule
```

TESTBENCH CODE:

```

module dff_test;
reg d,clk;
wire q,qd;
dff dff1(d,q,qd,clk);
initial
clk=1'b0;
always
#10 clk=~clk;
Initial
begin
$monitor($time,"q=%d","qd=%d",q,qd);
d=1'b0;
#30 d=1'b1;
#30 d=1'b0;
#30 $finish;
end
endmodule

```

 

JK FLIPFLOP**VERILOG CODE:**

```

module jkff(q,qb,clk,j,k,rst);
input clk,rst,j,k;
output q,qb;
reg q,tq;
always@ (posedge clk or posedge rst)
begin
if(rst==1)
begin
q<=1'b0;
tq<=1'b0;
end
else
begin
if(j==1'b1 && k==1'b0)
q<=j;
else if(j==1'b0 && k==1'b1)
q<=1'b0;
else if(j==1'b1 && k==1'b1)
begin
tq<=~tq;
q<=tq;
end
end
end
assign
qb=~q;
endmodule


```

TESTBENCH CODE:

```

module jk_test;
reg clk, rst,j,k;
wire q,qb;
jkff jk1(q,qb,clk,rst,j,k);
initial
clk =1'b0;
always
#10 clk=~clk;
initial
begin
j=1'b0;k=1'b0;rst=1'b0;
#30 rst=1'b0;
#60 j=1'b0;k=1'b1;
#20 j=1'b1;k=1'b0;
#20 j=1'b0;k=1'b1;
#20 j=1'b1;k=1'b1;
#50 rst=1'b1;
End
initial
#300 $finish;
endmodule

```

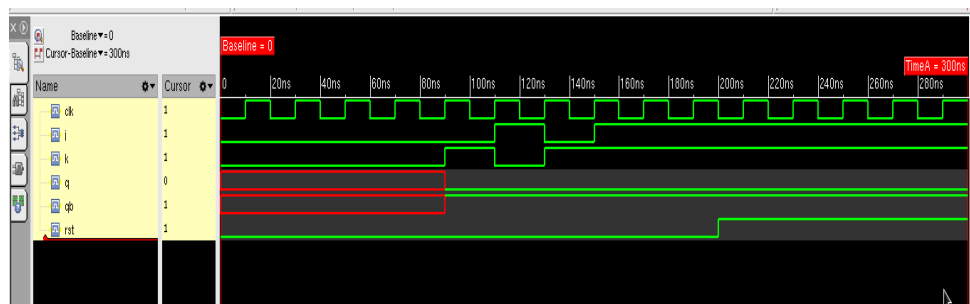

MS FLIPFLOP**VERILOG CODE:**

```

module msff(j,k,clk,q,qb);
input clk,j,k;
output q,qb;
reg q,qb,tq;
always@(clk)
begin
if(!clk)
begin
if(j==1'b0 && k==1'b1)
tq<=1'b0;
else if(j==1'b1 && k==1'b0)
tq<=1'b1;
else if(j==1'b1 && k==1'b1)
tq<=~tq;
end
if(clk)
begin
q<=tq;
qb<=~tq;
end
end
endmodule

```

TESTBENCH CODE:

```


module msff_test;
reg j,k,clk;
wire q,qb;
msff ms(j,k,clk,q,qb);
initial
clk=1'b0;
always

```

```

#10 clk=~clk;
initial
begin
j=1'b0;k=1'b0;
#60 j=1'b0;k=1'b1;
#40 j=1'b1;k=1'b0;
#20 j=1'b1;k=1'b1;
#40 j=1'b1;k=1'b0;
#5 jj=1'b0;k=1'b0;
#20 j=1'b1;
#10;
end
initial
#200 $finish;
endmodule

```

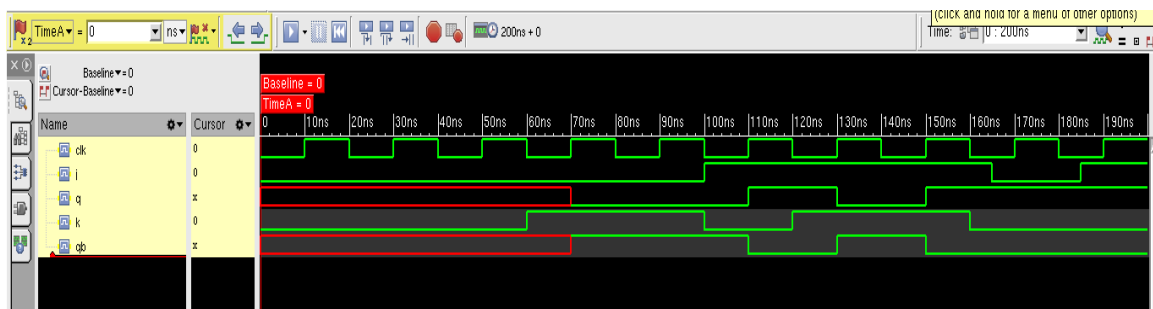

T FLIPELOP

VERILOG CODE:

```


module tff(q,qd,clk,rst,tin);
input tin,clk,rst;
output q,qd;
reg tq;
always@(posedge clk or posedge rst)
begin
if(rst==1)
tq<=1'b0;
else

```

```
begin
if(tin)
tq<=1'b1;
end
end
assign q=tq;
assign qb=~tq;
endmodule
```

TESTBENCH CODE:

```
module tff_test;
reg tin,rst,clk;
wire q,qd;
tff abc(q,qd,clk,rst,tin);
initial
clk=1'b0;
always
#10 clk=~clk;
initial
begin
rst=1'b1;tin=1'b0;
#300 rst=1'b0;
#100 tin=1'b1;
#205 tin=1'b0;
#300 tin=1'b1;
#175 tin=1'b0;
#280 rst=1'b1;
#200 rst=1'b0;
#280 tin=1'b1;
#100;
end
initial
#2000 $finish;
Endmodule
```

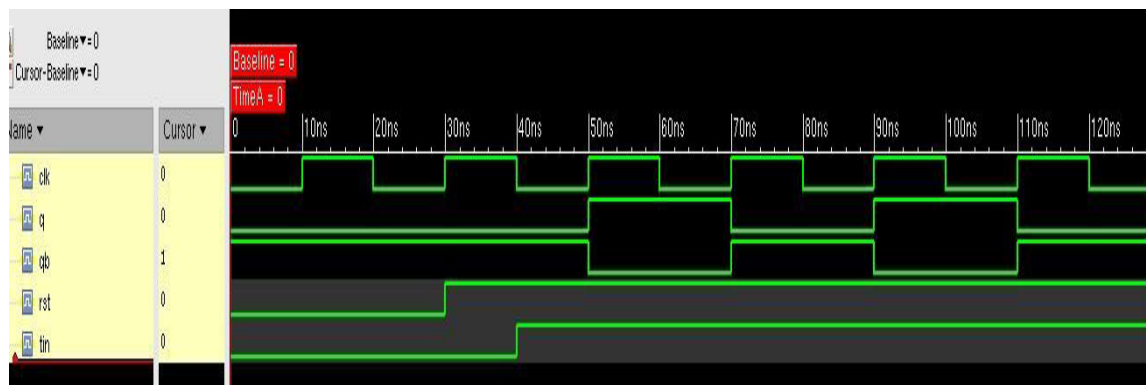1.8 Discussions:

1.9 Pre – Experimentation Questions:

1. What is Latch?
2. Discuss different types of memory.
3. Write the truth table for D & JK flip flop.
4. Write the truth table for MS, T flip flop.
5. Write the truth table for RS flip flop.

1.10 Post – Experimentation Questions:

1. Working of T flip-flops.
2. Discuss the difference of all the flip-flop mentioned.
3. Explain the working of D flip flop.
4. Explain the working of RS flip flop.
5. Explain the working of T and MS flip flop.

vi) Serial & Parallel Adder

1.1 Objective	1.6 Observation
1.2 Apparatus Required	1.7 Results
1.3 Pre-Requisite	1.8 Discussions
1.4 Introduction	1.9 Pre-Requisite Question
1.5 Procedure	1.10 Post-Requisite

1.1 Objectives:

To write a Verilog and test bench code for Adder and verify the output waveform.

1.2 Apparatus Required:

Cadence Tools.

1.3 Pre-Requisite:

Knowledge of full adder, half adder, binary addition.

1.4 Introduction:

The serial binary adder or bit-serial adder is a digital circuit that performs binary addition bit by bit. The serial full adder has three single-bit inputs for the numbers to be added and the carry in. Parallel adder is a combinatorial circuit (not clocked, does not have any memory and feedback) adding every bit position of the operands in the same time. Thus it is requiring number of bit-adders (full adders + 1 half adder) equal to the number of bits to be added.


1.5 Procedure:

1. Login to **redhat** operating system with the respective login name and password provided in the lab.
2. Right click on the screen and select **Open Terminal** to open the command prompt.
3. To enter into csh shell type **csh** in the command line.
4. To source the cadence tools type **source /cshrc/cad** in the command line.

STEPS TO COMPLETE AND SIMULATE THE VERILOG CODES

5. The Verilog code and test bench code should be written inside the respected directory
6. To write the Verilog code open the editor by typing **gedit<filename.v>** Eg: **gedit adder.v**.

 7. To write the test_bench code open the editor by typing **gedit<filename_test.v>**
Eg:**gedit. adder_test.v.**
8. To compile the verilog program **type ncvlog –mess <filename.v>**, check for errors.
9. To compile the test bench program **type ncvlog –mess <filename_test.v>**, check for errors.
10. To verify and run the verilog code in the cadence tool type **nclaunch –new** in terminal window.
11. Select **Single Step (IRUN only)**



12. Now the tool will verify the codes one by one and open a simulation window if there is no error.
13. Double click on the files both test and code files to check for errors.
14. Double click on the launch IRUN with current selection.
15. A new window will appear and in that select in and out right click on it and select the option **send to waveform.**
16. Verify the output.
17. To synthesize the verilog code type **rc –gui** in terminal window.
18. Once enter into gui window type the following commands.
19. **set_attr lib_search_path <copy and paste the library folder path>**

20. **set_attr library** <copy and paste the slow.lib file path inside the library folder>
21. **set_attr hdl_search_path** <copy and paste the verilog folder path>
22. **read_hdl** <filename.v>
23. **elaborate**
24. Once elaboration done synthesize the code by typing **synthesize** in terminal window.
25. Once synthesize done check for report power, area and gate
26. Optimize the program using command **synthesize –to_mapped**, and check for report power, area and gate. Compare the report of after and before optimization. Repeat same steps for all the programs.

1.6 Program:

VERILOG CODE:

```

module par(cin,x,y,sum,cout);
input cin;
input [3:0]x,y;
output[3:0]sum;
output cout;
fulladd g0(cin,x[0],y[0],sum[0],c0);
fulladd g1(c0,x[1],y[1],sum[1],c1);
fulladd g2(c1,x[2],y[2],sum[2],c2);
fulladd g3(c2,x[3],y[3],sum[3],cout);
endmodule

module fulladd(cin,x,y,sum,cout);
input cin ,x,y;
output sum ,cout;
assign sum=x^y^cin;
assign cout=((x&y)||(x&cin)||(y&cin));
endmodule

```

TESTBENCH CODE:

```

module par_test;
reg [3:0]x,y;


```

```

reg cin;
wire [3:0]sum;
wire cout;
par abc(cin,x,y,sum,cout);
initial
begin
$monitor($time,"sum=%d",sum);
x=4'b0000;y=4'b0000;
cin=1'b0;
#20 x=4'b1111;y=4'b1010;
#20 x=4'b1011;y=4'b0110;
#20 x=4'b1111;y=4'b1111;
#50 $finish;
end
endmodule

```

1.7 Results :

 

1.8 Discussions:

1.9 Pre – Experimentation Questions:

1. Discuss half adder.
2. Discuss full adder.
3. Explain the binary addition.
4. Explain 2's complement
5. Explain binary subtraction.

1.10 Post – Experimentation Questions:

1. Explain working of serial adder
2. Explain working of parallel adder.
3. Explain the waveform generated by the code.
4. Explain the difference between serial and parallel adder.
5. Explain the verilog code for the same.

vii) 4 bit Counter (Synchronous and Asynchronous Counter)

1.1 Objective	1.5 Observation
1.2 Apparatus Required	1.7 Results
1.3 Pre-Requisite	1.8 Discussions
1.4 Introduction	1.9 Pre-Requisite Question
1.5 Procedure	1.10 Post-Requisite

1.1 Objectives:

To write a Verilog and test bench code for Counter and verify the output waveform.

1.2 Apparatus Required:

Cadence Tools.

1.3 Pre-Requisite:

Basic knowledge of binary counters and difference between synchronous and asynchronous.

1.4 Introduction:

In an **asynchronous counter**, an external event is used to directly SET or CLEAR a flip-flop when it occurs. In a **synchronous counter** however, the external event is used to produce a pulse that is synchronised with the internal clock. An example of an **asynchronous counter** is a **ripple counter**.


1.5 Procedure:

1. Login to **redhat** operating system with the respective login name and password provided in the lab.
2. Right click on the screen and select **Open Terminal** to open the command prompt.
3. To enter into csh shell type **csh** in the command line.
4. To source the cadence tools type **source /cshrc/cad** in the command line.

STEPS TO COMPLETE AND SIMULATE THE VERILOG CODES

5. The Verilog code and test bench code should be written inside the respected directory
6. To write the Verilog code open the editor by typing **gedit<filename.v>** Eg:**gedit counter.v**.
7. To write the test_bench code open the editor by typing **gedit<filename_test.v>** Eg:**gedit. counter_test.v**.

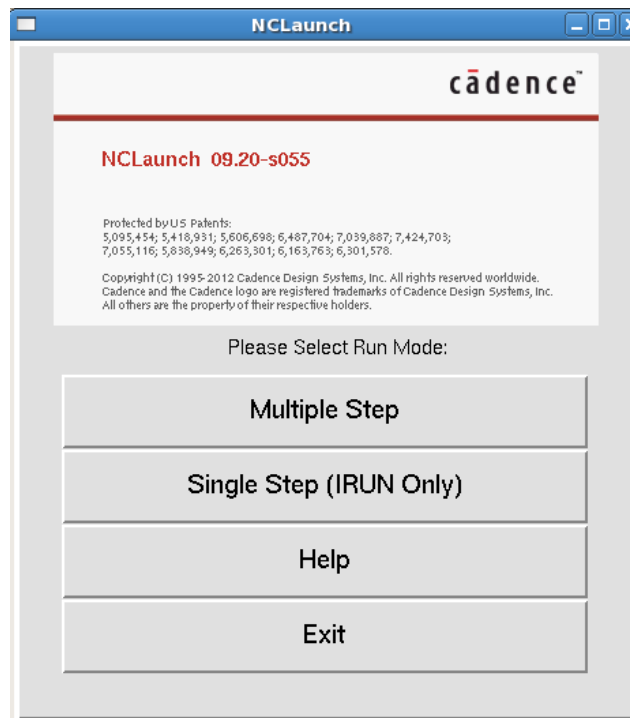8. To compile the verilog program type **ncvlog –mess <filename.v>**, check for errors.
9. To compile the test bench program type **ncvlog –mess <filename_test.v>**, check for errors.
10. To verify and run the verilog code in the cadence tool type **nclaunch –new** in terminal window.
11. Select **Single Step (IRUN only)**



12. Now the tool will verify the codes one by one and open a simulation window if there is no error.
13. Double click on the files both test and code files to check for errors.
14. Double click on the launch IRUN with current selection.
15. A new window will appear and in that select in and out right click on it and select the option **send to waveform**.
16. Verify the output.
17. To synthesize the verilog code type **rc –gui** in terminal window.
18. Once enter into gui window type the following commands.
19. **set_attr lib_search_path <copy and paste the library folder path>**
20. **set_attr library <copy and paste the slow.lib file path inside the library folder>**
21. **set_attr hdl_search_path <copy and paste the verilog folder path>**

22. read_hdl <filename.v>
23. elaborate
24. Once elaboration done synthesize the code by typing **synthesize** in terminal window.
25. Once synthesize done check for report power, area and gate
26. Optimize the program using command **synthesize –to_mapped**, and check for report power, area and gate. Compare the report of after and before optimization. Repeat same steps for all the programs.

1.6 Program:

SYNCHRONOUS COUNTER

VERILOG CODE:

```

module syncnt(cnt,e,q);
input cnt,e;
output [3:0]q;
wire e1,e2,e3;
tff aa(e,cnt,q[0]);
and1 go(q[0],e,e1);
tff bb(e1,cnt,q[1]);
and2 g1(q[1],q[0],e,e2);
tff cc(e2,cnt,q[2]);
and3 g2(q[2],q[1],q[0],e,e3);
tff dd(e3,cnt,q[3]);
endmodule

module tff(t,clk,q);
input t,clk;
output q;
reg q;
initial
q=1'b0;
always@(posedge clk)
begin
if(t==0)

```

```
q=q;
else
q=~q;
end
endmodule

module and1(a,b,c);
input a,b;
output c;
assign c=a&b;
endmodule


module and2(d,e,f,g);
input d,e,f;
output g;
assign g=d&e&f;
endmodule

module and3(p,q,r,s,t);
input p,q,r,s;
output t;
assign t=p&q&r&s;
endmodule
```

TESTBENCH CODE:

```
module syncnt_test;
reg cnt,e;
wire[3:0]q;
syncnt a1(cnt,e,q);
initial
begin
cnt=0;
e=1;
end
always #10cnt=~cnt;
endmodule
```

1.7 Results :

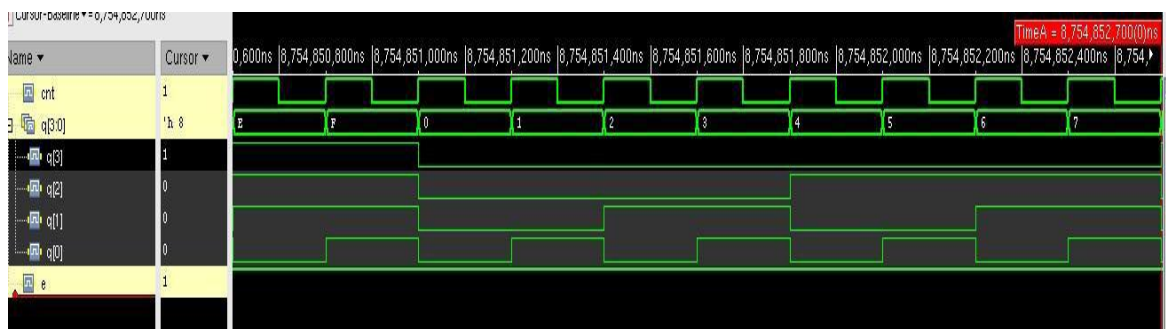

ASYNCHRONOUS COUNTER

VERILOG CODE:

```

module account(cnt,e,q);
input cnt,e;
output [3:0]q;
wire q1,q2,q3,q4;
tff aaa(e,cnt,q[0],q1);
tff bbb(e,q1,q[1],q2);
tff ccc(e,q2,q[2],q3);
tff ddd(e,q3,q[3],q4);
endmodule

module tff(t,clk,q,qb);
input t,clk;
output q,qb;
reg q,qb;
initial
begin
q=1'b0;
qb=1'b1;
end
always@(posedge clk)
begin
if(t==0)
q=q;

```

```

else
q=~q;
qb=~q;
end
endmodule


```

TESTBENCH CODE:

```

module account_test;
reg cnt,e;
wire [3:0]q;
account ac(cnt,e,q);
initial
begin
cnt=0;
e=1;
end
always
#100 cnt=~cnt;
Endmodule

```

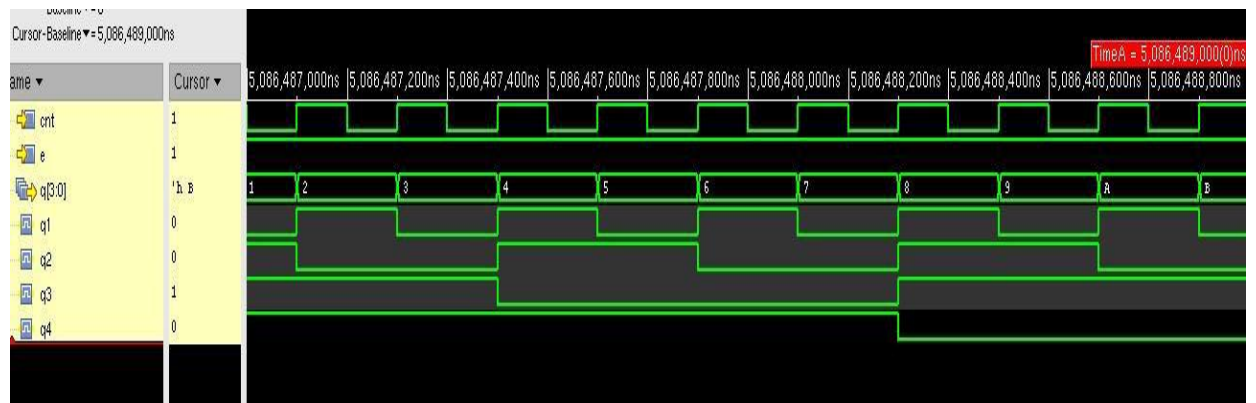

1.8 Discussions:

1.9 Pre – Experimentation Questions:

1. Explain ripple counter.
2. Explain binary counter.
3. Explain modulo counters.
4. What is the difference between ripple and binary counter.
5. What is the difference between synchronous and asynchronous in digital circuit.

1.10 Post – Experimentation Questions:

1. Explain the working of synchronous counter.
2. Explain the working of asynchronous counter.
3. Explain the waveform generated by synchronous counter.
4. Explain the waveform generated by asynchronous counter.
5. Explain the verilog code for the same.

viii) Successive Approximation Register (SAR)

1.1 Objective	1.6 Observation
1.2 Apparatus Required	1.7 Results
1.3 Pre-Requisite	1.8 Discussions
1.4 Introduction	1.9 Pre-Requisite Question
1.5 Procedure	1.10 Post-Requisite

1.1 Objectives:

To write a Verilog and test bench code for SAR and verify the output waveform.

1.2 Apparatus Required:

Cadence Tools.

1.3 Pre-Requisite:

Knowledge of ADC, Registers.

1.4 Introduction:

Successive Approximation ADC. Successive approximation ADC is the advanced version of Digital ramp type ADC which is designed to reduce the conversion and to increase speed of operation. The successive approximation register counts by changing the bits from MSB to LSB according to input.


1.5 Procedure:

1. Login to **redhat** operating system with the respective login name and password provided in the lab.
2. Right click on the screen and select **Open Terminal** to open the command prompt.
3. To enter into csh shell type **csh** in the command line.
4. To source the cadence tools type **source /cshrc/cad** in the command line.

STEPS TO COMPLETE AND SIMULATE THE VERILOG CODES

5. The Verilog code and test bench code should be written inside the respected directory
6. To write the Verilog code open the editor by typing **gedit<filename.v>** Eg:**gedit sar.v.**
7. To write the test_bench code open the editor by typing **gedit<filename_test.v>** Eg:**gedit. sar_test.v.**

 8. To compile the verilog program **type nclog -mess <filename.v>**, check for errors.
9. To compile the test bench program **type nclog -mess <filename_test.v>**, check for errors.
10. To verify and run the verilog code in the cadence tool type **nclaunch -new** in terminal window
11. Select **Single Step (IRUN only)**



12. Now the tool will verify the codes one by one and open a simulation window if there is no error.
13. Double click on the files both test and code files to check for errors.
14. Double click on the launch IRUN with current selection.
15. A new window will appear and in that select in and out right click on it and select the option **send to waveform**.
16. Verify the output.
17. To synthesize the verilog code type **rc -gui** in terminal window.
18. Once enter into gui window type the following commands.
19. **set_attr lib_search_path <copy and paste the library folder path>**
20. **set_attr library <copy and paste the slow.lib file path inside the library folder>**

21. set_attr hdl_search_path <copy and paste the verilog folder path>
22. read_hdl <filename.v>
23. elaborate
24. Once elaboration done synthesize the code by typing **synthesize** in terminal window.
25. Once synthesize done check for report power, area and gate
26. Optimize the program using command **synthesize –to_mapped**, and check for report power, area and gate. Compare the report of after and before optimization. Repeat same steps for all the programs.

1.6 Program:

VEROLIG CODE:

```

module sar(l,e,w,clk,r,q);
input l,e,w,clk;
input [3:0]r;
output [3:0]q;
reg [3:0]q;
integer k;
always@(posedge clk)
if(1)
q=r;
else if(e)
begin
for(k=0;k<3;k=k+1)
q[k]=q[k+1];
q[3]=w;
end
endmodule

```

TESTBENCH CODE:

```

module sar_test;
reg l,e,w,clk;
reg [3:0]r;
wire [3:0]q;

```




```

sar abc(l,e,w,clk,r,q);
initial
clk=1'b0;
always
#10 clk=~clk;
initial
begin
l=1'b1;
w=1'b0;
e=1'b0;
#5 r=4'b1111;
#10 l=1'b0;e=1'b1;w=1'b0;
#10 w=1'b0;
#10 w=1'b0;
#10 w=1'b0;
#10 w=1'b0;
#10 w=1'b1;
#10 w=1'b1;
#10 w=1'b1;
#10 w=1'b1;
#10 $finish;
end
endmodule

```

1.7 Results :

 

1.8 Discussions:**1.9 Pre – Experimentation Questions:**

1. What is sampling.
2. What is sampling theorem.
3. Explain R-2R DAC.
4. Explain working of ADC
5. Explain working of DAC.

1.10 Post – Experimentation Questions:

1. Discuss successive approximation register.
2. Explain functioning of ADC in detail.
3. Explain the verilog code for SAR.
4. Explain the waveforms generated by the same.
5. Define Nyquist rate.

EXPERIMENT No. 01: Design an Inverter with given specifications, completing the design flow mentioned below:**

a. Draw the schematic and verify the following

i) DC Analysis ii) Transient Analysis

b. Draw the Layout and verify the DRC, ERC

c. Check for LVS

d. Extract RC and back annotate the same and verify the Design

e. Verify & Optimize for Time, Power and Area to the given constraint*

1.1 Objective	1.6 Observation
1.2 Apparatus Required	1.7 Results
1.3 Pre-Requisite	1.8 Discussions
1.4 Introduction	1.9 Pre-Requisite Question
1.5 Procedure	1.10 Post-Requisite

1.1 Objectives:

Design an Inverter with given specifications and complete design till layout and verify the parameters DRC, ERC, QRC. Extract RC and back annotate for the verification.

1.2 Apparatus Required:

Cadence Tools.

1.3 Pre-Requisite:

Basic Knowledge of CMOS and MOSFET. W/L ratio.

1.4 Introduction:

It consists of PMOS and NMOS FET. The input A serves as the gate voltage for both transistors. The NMOS transistor has an input from Vss (ground) and PMOS transistor has an input from Vdd. The terminal Y is output. When a high voltage ($\sim V_{dd}$) is given at input terminal (A) of the inverter, the PMOS becomes open circuit and NMOS switched OFF so the output will be pulled down to Vss.


When a low-level voltage ($< V_{dd}$, $\sim 0V$) applied to the inverter, the NMOS switched OFF and PMOS switched ON. So the output becomes Vdd or the circuit is pulled up to Vdd.

A CMOS circuit is composed of two MOSFETs. The top FET is a PMOS type device while the bottom FET is an NMOS type. The body effect is not present in either device since the body of each device is directly connected to the device's source. Both gates are connected to the input line. The output line connects to the drains of both FETs.

 1.5 Procedure:


STEPS FOR THE ANALOG LAB

- Login to **redhat** operating system with the respective login name and password provided in the lab.
- Right click on the screen and select **Open Terminal** to open the command prompt.
- To enter into csh shell type **csh** in the command line.
- To source the cadence tools type **source /cshrc/cad** in the command line.
- To open the tool type **virtuoso &** in the command line.




Creating the Library

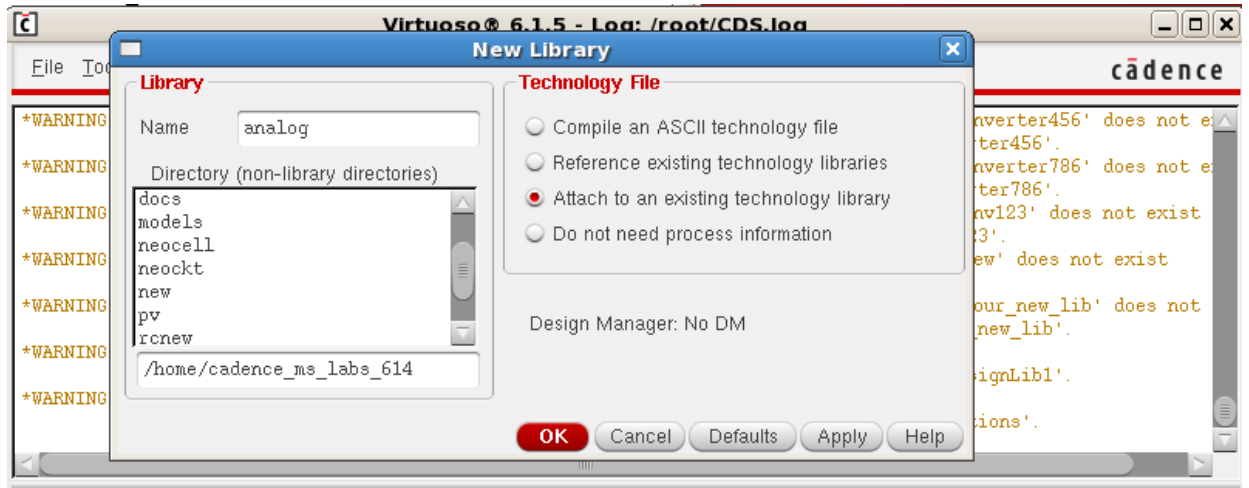- Creating a new library by going to the link **File -> New -> Library**
- Give the library name and click ok.
- Select **attach to an existing technology library** and click **ok**.




- Select **gpdK180** and click **ok**.

 


SCHEMATIC AND SYMBOL CREATION

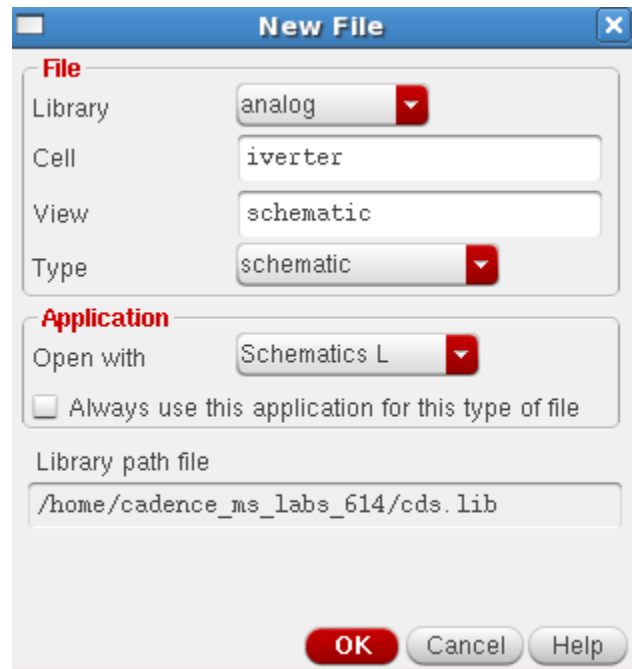
- In the Library manager select given library
- In Library manager select **File -> New -> Cell view**.
- Give the cell name as inverter



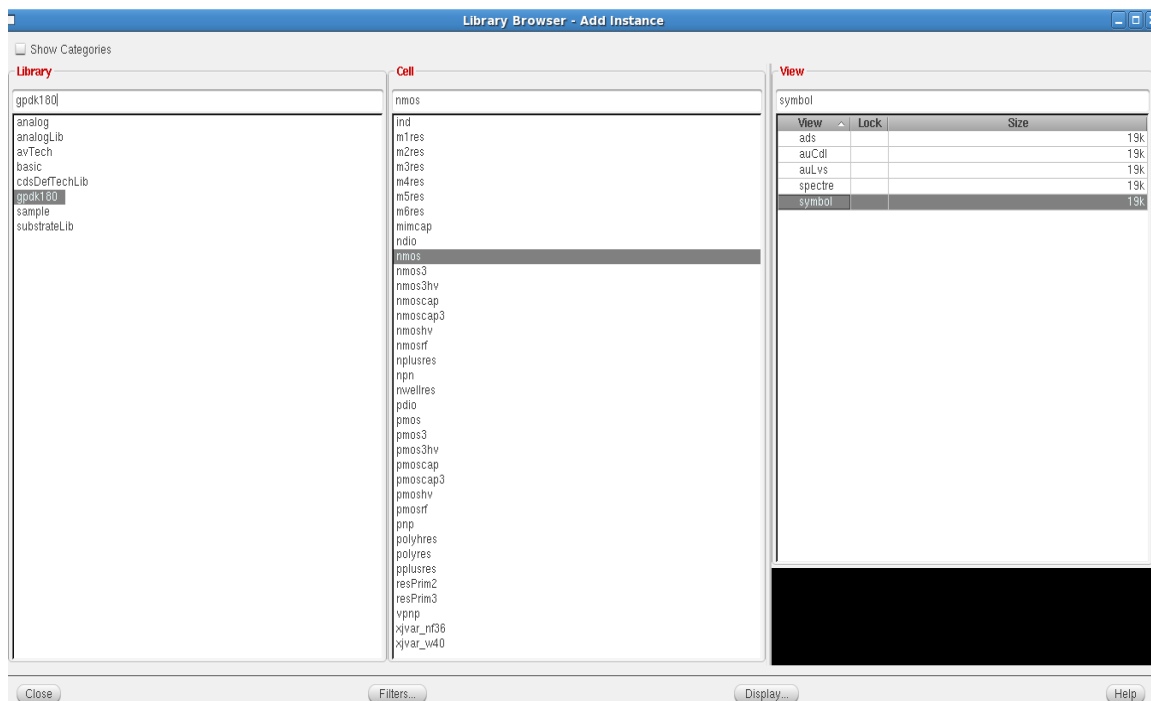- Virtuoso Schematic Editor will open.
- Select Create -> Instance, and select the required components (pmos & nmos symbols)



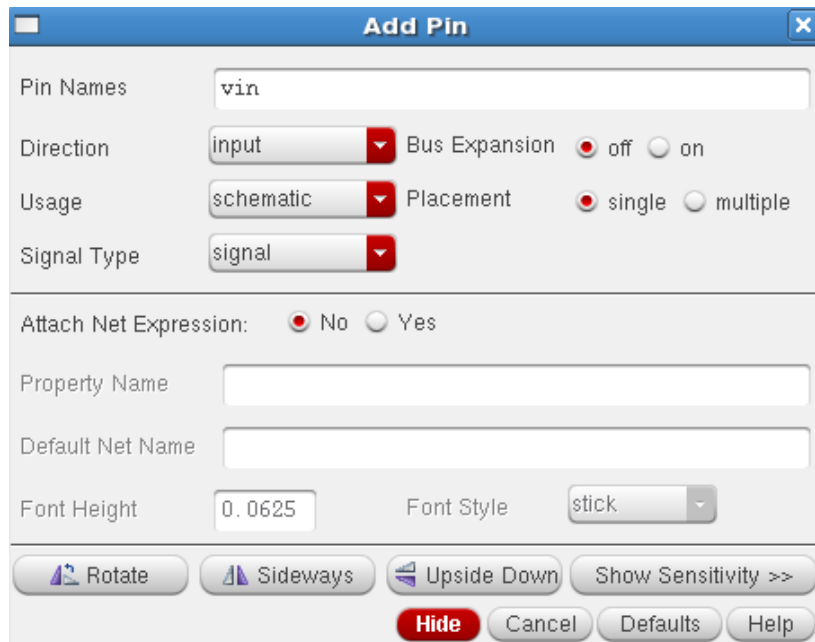
- Select **Create -> pins**, and place the ports (vin, vdd, gnd, vout) on the editor.




- Make the complete connection by using wires by selecting **create -> wire (narrow)**
- After complete of the schematic, save the file by **file -> check & save**


1.6 Observations:

SCHEMATIC:

 

 
SYMBOL:

- To create symbol **Create -> Cell View -> From Cell view.**
- Virtuoso symbol editor opens.
- Place the right, left, bottom and top pins.
- Create shape of the cell using option in **Create -> Shapes.**

 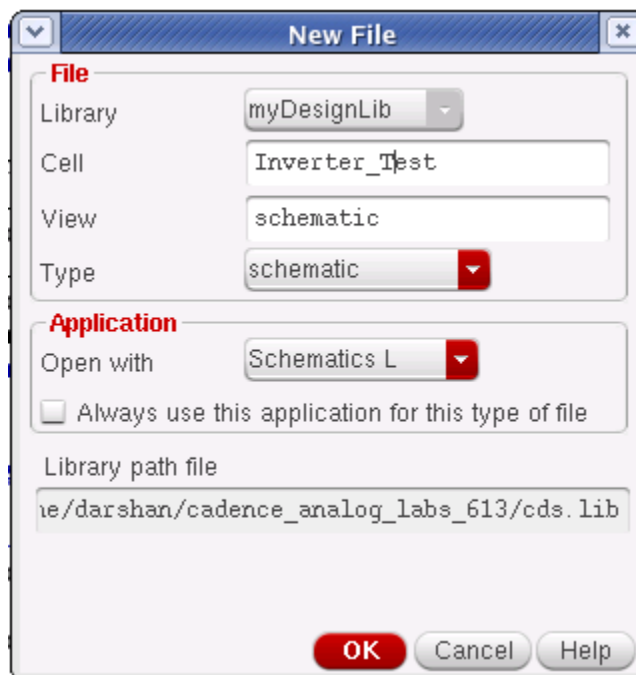**BUILDING THE TEST DESIGN FOR THE CELL**


- In the library manager select given library

- Select **File -> New -> Cell view**.
- Give the cell name as **inverter_test**.




- Virtuoso Schematic editor window will open.
- Select **create -> instance**, and select the design to test.
- To apply inputs, **create -> instance**. In the library select **analoglib** and select appropriate inputs (vpulse, vdc, gnd).


Library name	Cellview name	Properties/Comments
Scem	Inverter	Symbol
analogLib	vpulse	v1=0, v2=1.8, td=0 tr=tf=1ns, ton=10n, T=20n
analogLib	vdc, gnd	vdc=1.8

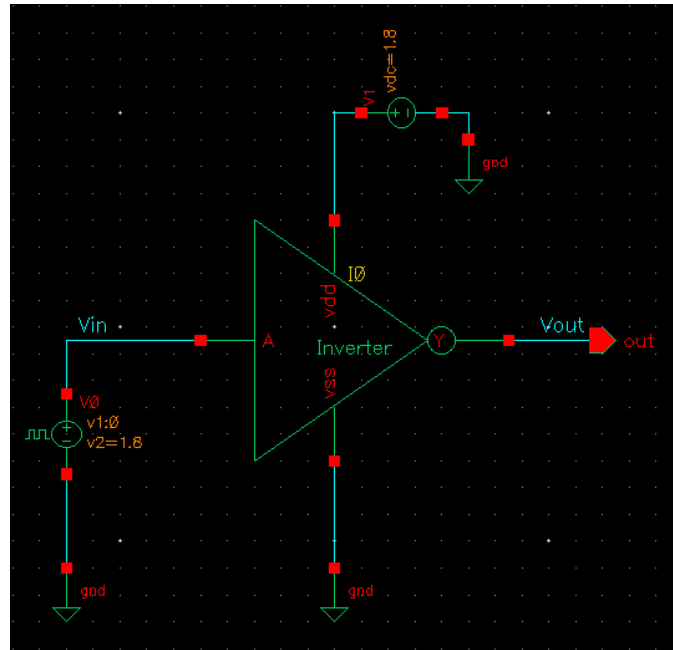



STEPS TO SIMULATE

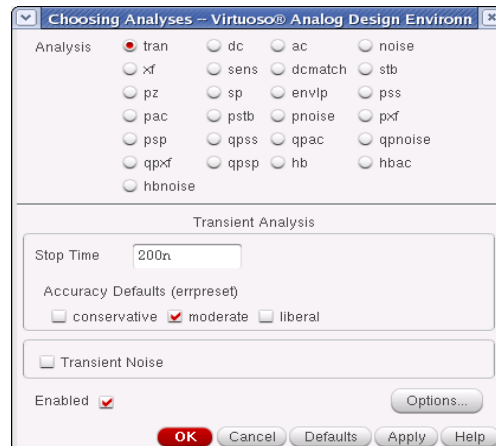- In the Virtuoso Schematic Editor after completing the test circuit design **launch->ADEL**
- Virtuoso Analog Design Environment window opens.
- Go to **Analyses -> choose**, give appropriate inputs for **tran** for transient analyses and **dc** for dc analyses.




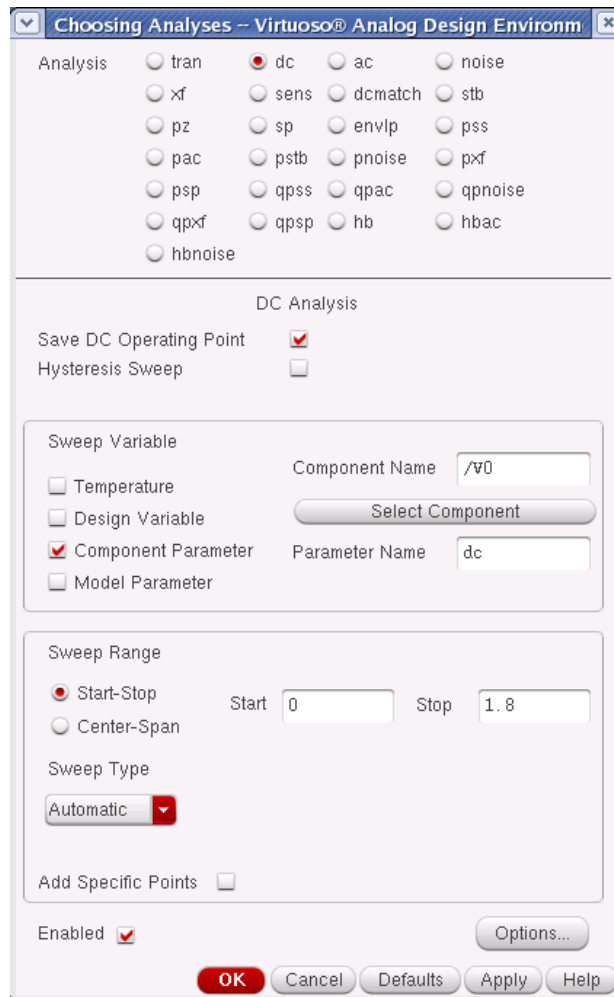

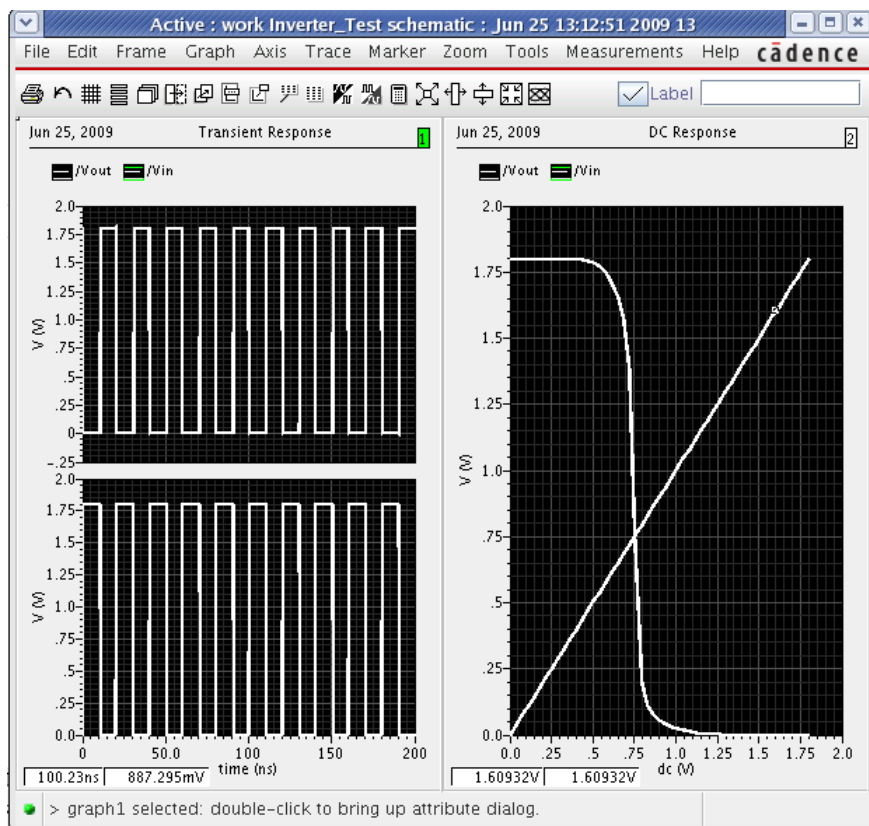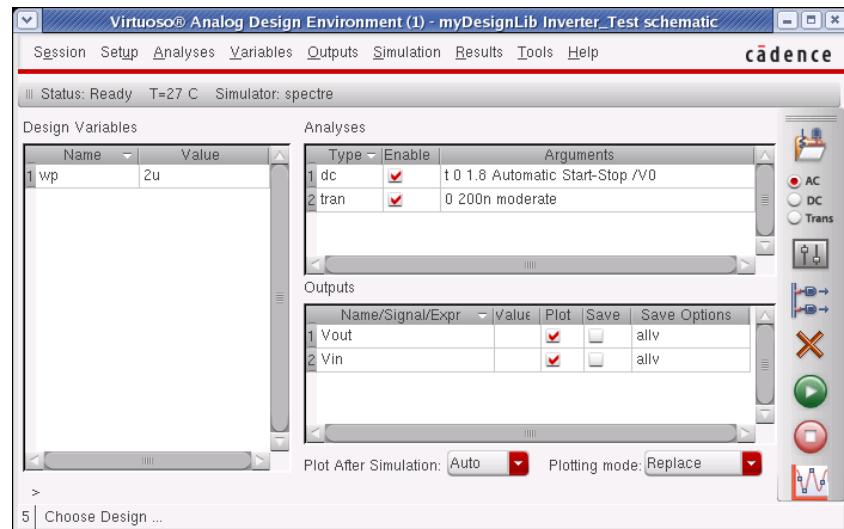- Go to **outputs -> to be plotted -> select on schematic** (input and output wires).
- Go to **simulation -> netlist and run**
- When simulation finishes, the Transient, DC plots automatically will be popped up along with log file.



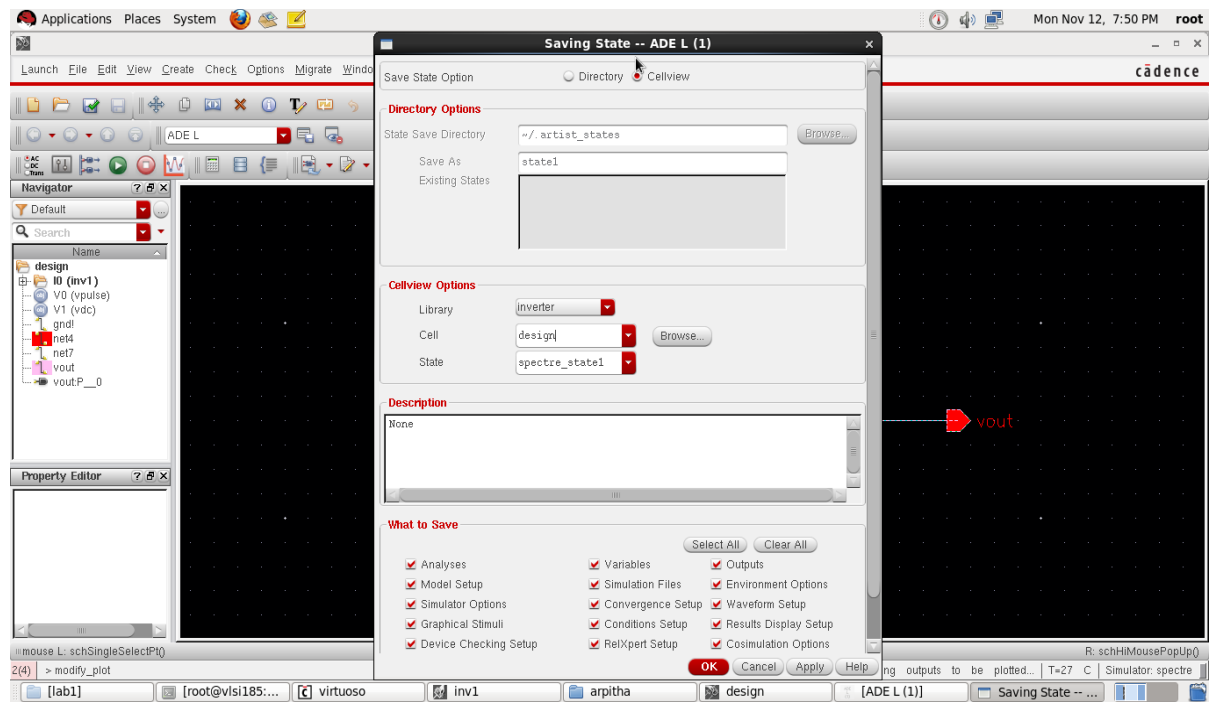
- To save the waveform, go to **session** in the ADEL window and in session select **save state**, under it click on **cell view** and then okay.



STEPS FOR CREATING LAYOUT VIEW


- From the **Inverter** schematic window menu execute **Launch – Layout XL**. A **Startup Option** form appears.
- Select **Create New** option. This gives a New Cell View Form
- Check the Cellname (**Inverter**), Viewname (**layout**).
- Click **OK** from the New Cellview form.
- LSW and a blank layout window appear along with schematic window.

Adding Components to Layout

- Execute **Connectivity – Generate – All from Source** or click the icon  in the layout editor window, **Generate Layout** form appears. Click **OK** which imports the schematic components in to the Layout window automatically.
- Re arrange the components with in PR-Boundary as shown in the next page.
- Press Shift –f in the layout window to display all the levels.
- To rotate a component, Select the component and execute **Edit –Properties**. Now select the degree of rotation from the property edit form.



 - To Move a component, Select the component and execute **Edit -Move** command.



PHYSICAL VERIFICATION


Select **Assura** → **technology** → **Browse** → click on previous directory(..) until we get a **cad** option → double click on **cad** → **foundary** → **analog** → **180nm** → **assura.tech.lib** → **okay**.

Assura DRC

Running a DRC

- Open the Inverter layout form the CIW or library manger if you have closed that.
- Select **Assura - Run DRC** from layout window.
- The DRC form appears. The Library and Cellname are taken from the current design window, but rule file may be missing. Select the Technology as **gpd180**. This automatically loads the rule file.

Your DRC form should appear like this

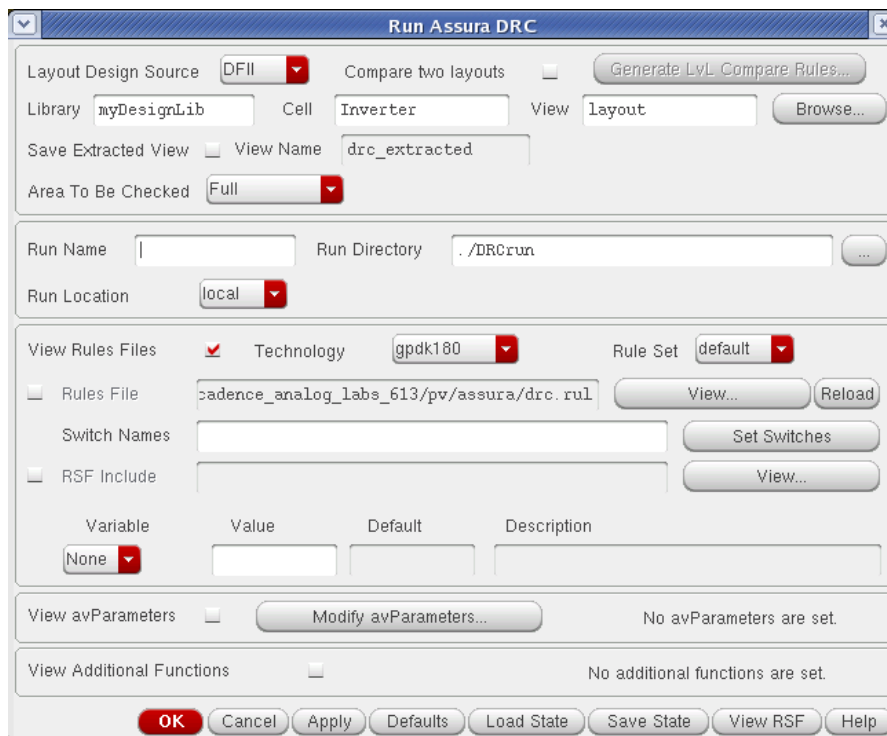

- Click **OK** to start DRC.
- A Progress form will appear. You can click on the watch log file to see the log file.
- When DRC finishes, a dialog box appears asking you if you want to view your DRC results, and then click **Yes** to view the results of this run.
- If there are any DRC errors in the design, the **View Layer Window (VLW)** and **Error Layer Window (ELW)** appear. Also, the errors highlight in the design itself.
- Click **View – Summary** in the ELW to find the details of errors.
- You can refer to the rule file also for more information, correct all the DRC errors and **Re-run** the DRC.
- If there are no errors in the layout, then a dialog box appears with **No DRC errors found** written in it, click on **close** to terminate the DRC run.

ASSURA LVS

In this section, we will perform the LVS check that will compare the schematic netlist and the layout netlist.

Running LVS

- Select **Assura – Run LVS** from the layout window.

The Assura Run LVS form appears. It will automatically load both the schematic and layout view of the cell.

- Change the following in the form and click OK.

- The LVS begins and a Progress form appears.
- If the schematic and layout matches completely, you will get the form displaying **Schematic and Layout Match**.
- If the schematic and layout do not matches, a form informs that the LVS completed successfully and asks if you want to see the results of this run.
- Click **Yes** in the form.

LVS debug form appears, and you are directed into LVS debug environment.

- In the **LVS debug form** you can find the details of mismatches and you need to correct all those mismatches and **Re – run** the LVS till you will be able to match the schematic with layout.



ASSURA RCX

In this section we will extract the RC values from the layout and perform analog circuit simulation on the designs extracted with RCX.


Before using RCX to extract parasitic devices for simulation, the layout should match with schematic completely to ensure that all parasites will be backannotated to the correct schematic nets.

Running QRC

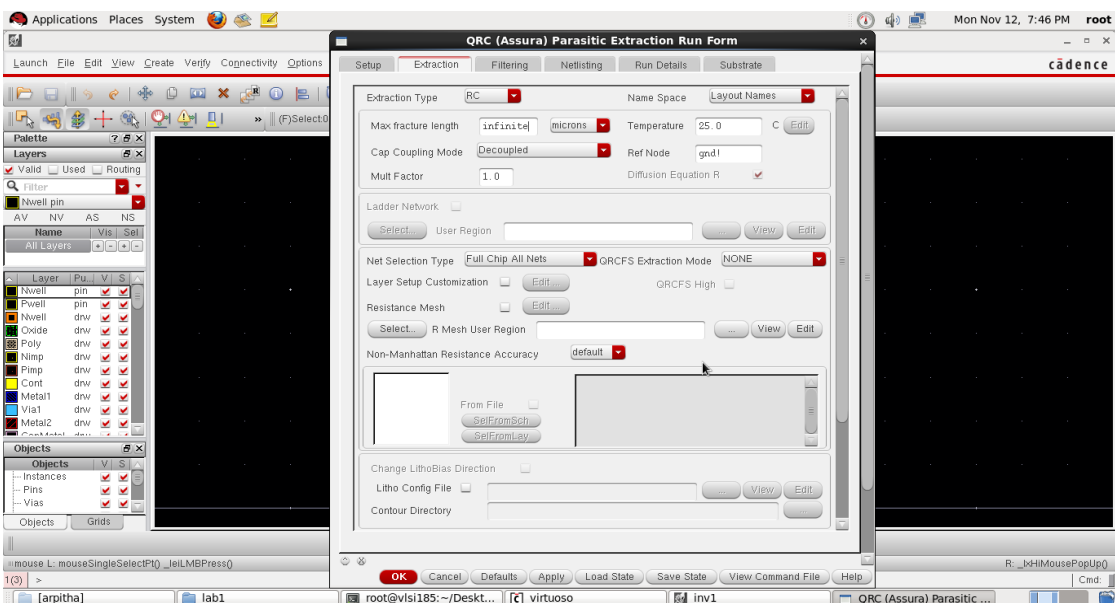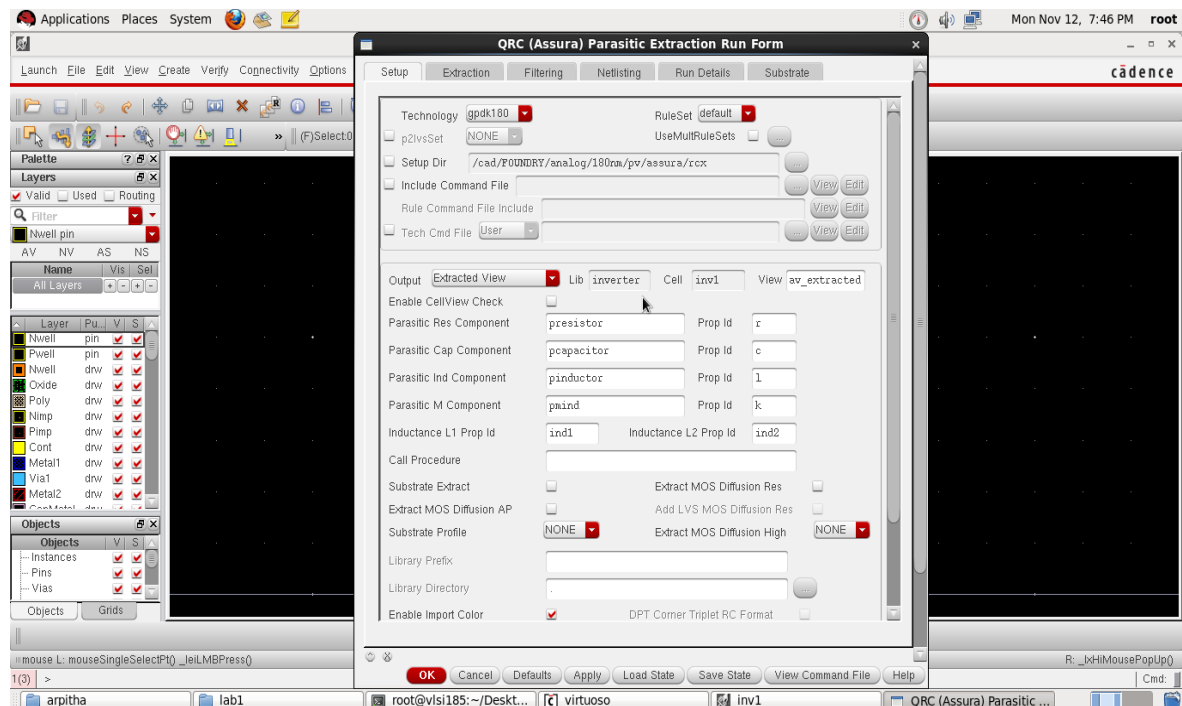- From the layout window execute **Assura – Run QRC**
- In QRC window, under **set up** option select **output as extracted view**,
- Under **Extraction** option, keep **extracted type as RC** and **ref node as gnd!** Or **vss!**




AvExtracted View

 


Steps to obtain Back Annotate Wave

 
- Select the given library name, and select the schematic test.



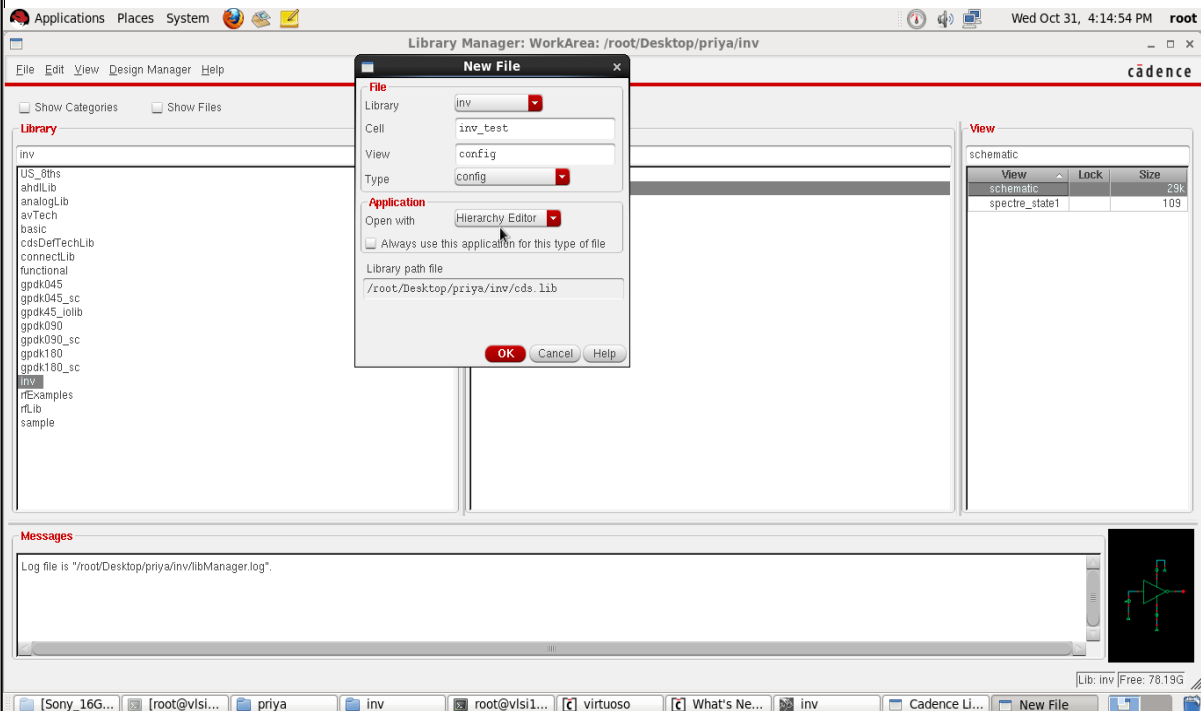
- Go to library manager, click on **New** → **cell view** → keep type as **config**



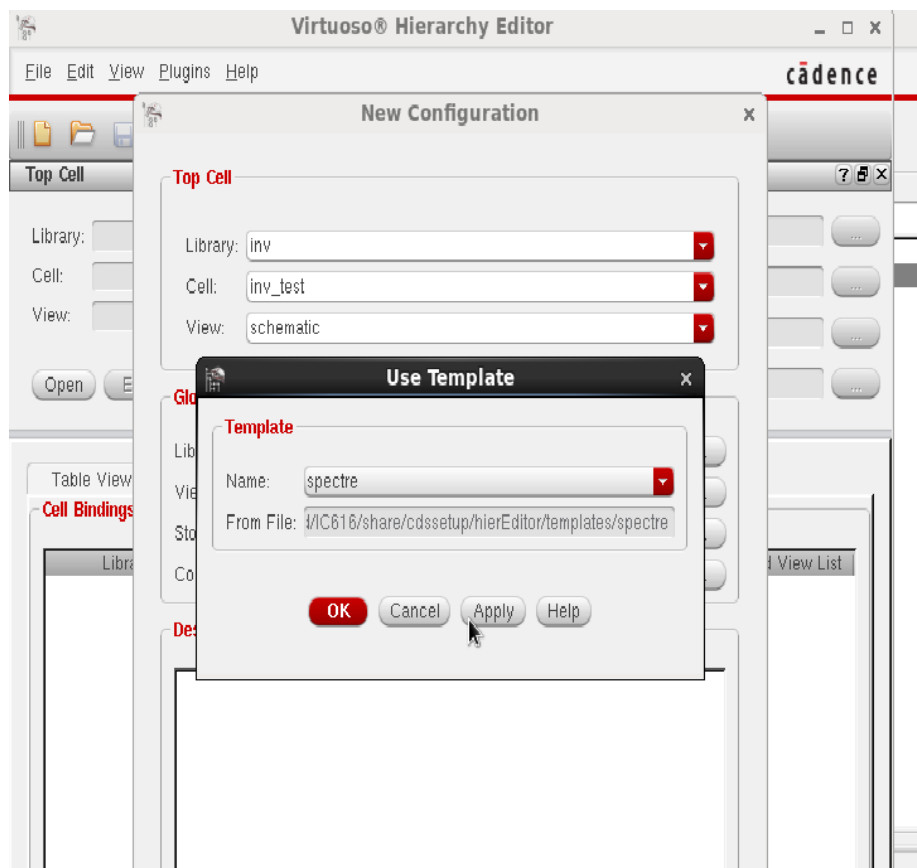
- Below window will appear, select **view as schematic** and select **use template**, under it select **spectre** → **okay**



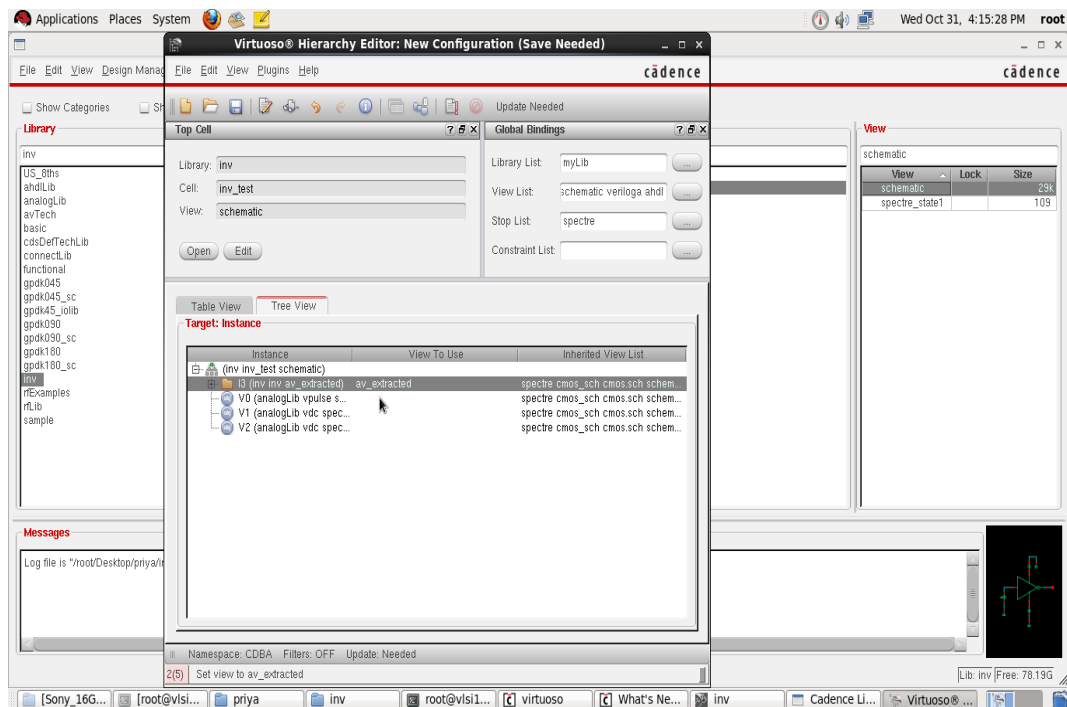- In Hierarchy editor window click on **Tree View**, right click on the folder, click on **av_extracted**.




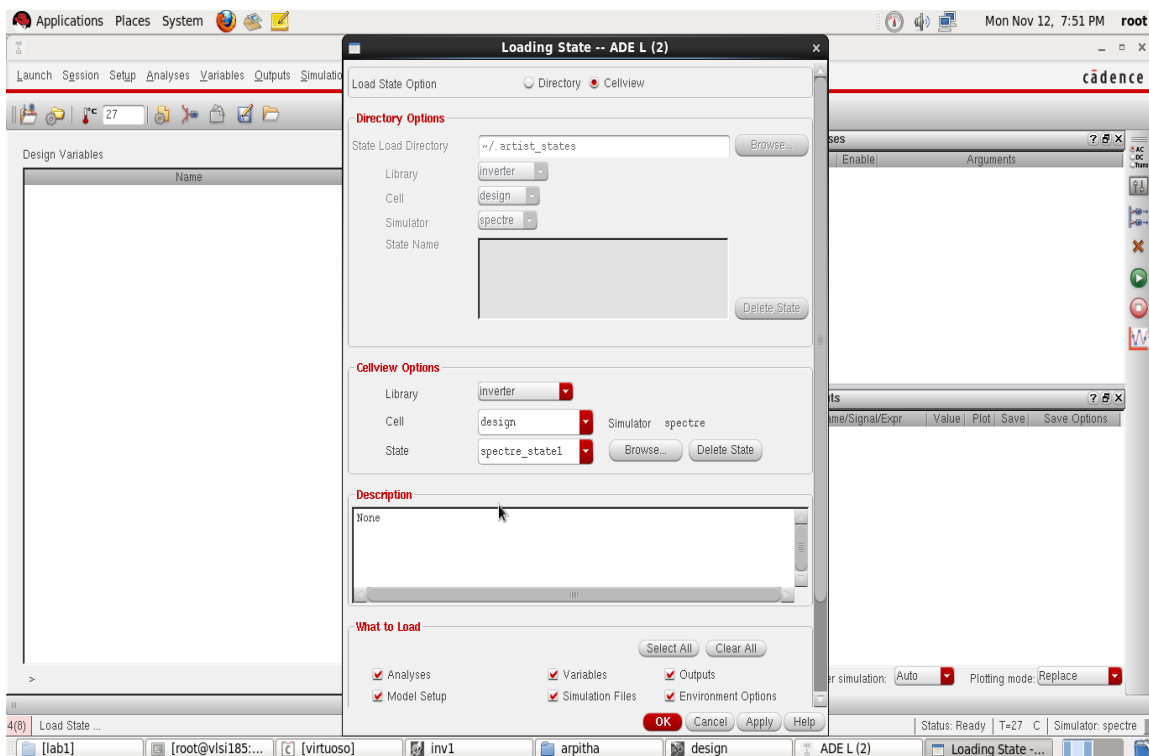- Click on Open→(schematic test window will be opened)→launch ADEL
- To load the simulated graph ,In ADEL Click on session →load state →cell view →okay



- Once the schematic waveform is loaded, Click on the run symbol in ADEL window to obtain back annotate wave.

1.7 Results :

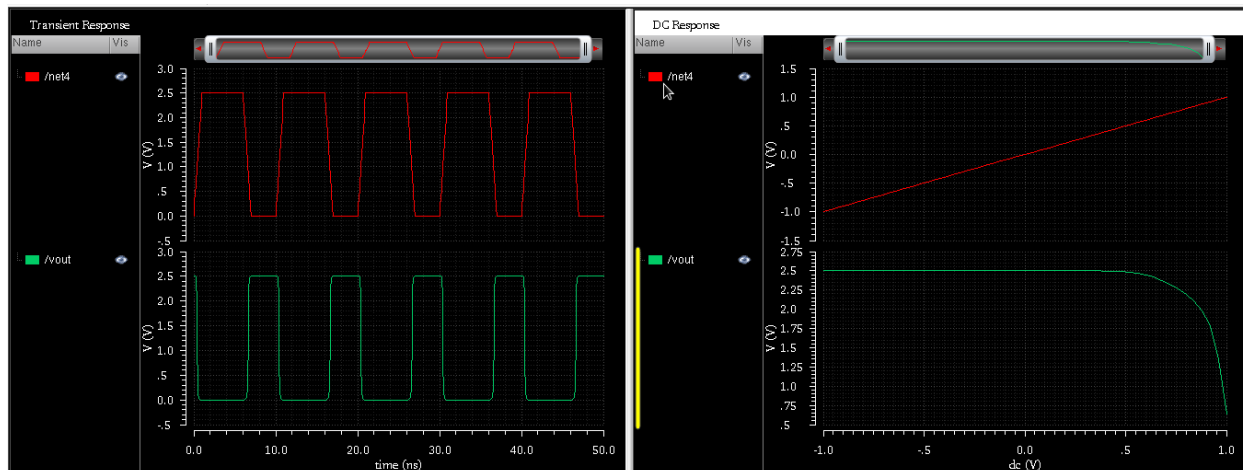

1.8 Discussions:

1.9 Pre – Experimentation Questions:

1. Explain MOSFET, CMOS
2. Explain W/L ratio.
3. What is gpdk.
4. What is body effect.
5. What are the different rules followed in LAYOUT design and what are the importance of the same.

1.10 Post – Experimentation Questions:

1. Explain the inverter characteristics transient response.
2. Explain the DC analysis of inverter.
3. What is the importance of DRC
4. What is ERC.
5. Discuss the need of back annotation.

EXPERIMENT No. 02: Design the (i) Common source and Common Drain amplifier and (ii) A Single Stage differential amplifier, with given specifications, completing the design flow mentioned below:**

a. Draw the schematic and verify the following

i) DC Analysis ii) AC Analysis iii) Transient Analysis

b. Draw the Layout and verify the DRC, ERC

c. Check for LVS

d. Extract RC and back annotate the same and verify the Design.

2.1 Objective

2.2 Apparatus Required

2.3 Pre-Requisite

2.4 Introduction

2.5 Procedure

2.6 Observation

2.7 Results

2.8 Discussions

2.9 Pre-Requisite Question

2.10 Post-Requisite

2.1 Objectives:

Design Common source, common drain and single stage differential amplifier with given specifications and complete design till layout and verify the parameters DRC, ERC, QRC. Extract RC and back annotate for the verification.

2.2 Apparatus Required:

Cadence Tools.

2.3 Pre-Requisite:

Knowledge of tool flow of cadence, design rules and working of amplifiers.

2.4 Introduction:

The common-source amplifier is one of the basic amplifiers in CMOS analog circuits. Because of its very high input impedance, relatively high gain, low noise, speed, and simplicity, common-source amplifiers find different applications from sensor signal amplification to RF low-noise amplification. Good understanding of this amplifier is essential not only for good design of one but also for analysis of other advanced circuits such as differential amplifiers.

A common-drain amplifier is one in which the input signal is applied to the gate and the output is taken from the source, making the drain common to both. Because it is

common, there is no need for a drain resistor. A common-drain amplifier is shown below. A common-drain amplifier is also called a source-follower. Self-biasing is used in this particular circuit. The input signal is applied to the gate through a coupling capacitor, and the output signal is coupled to the load resistor through the other capacitor.

The differential amplifier boosts the difference between the two input signals demonstrated as V_+ and V_- and rejects any common signals from the two sources. Its ideal characteristics are infinite bandwidth, gain, and common mode rejection ratio (CMRR); and high input impedance, less distortion, and low output admittance. It is also characterized to have less harmonic distortion and high output voltage swing. Its characteristics test the effective performance of the circuit. These amplifiers are broadly used in linear amplification circuits to obtain less distortion at the output. They can be designed in multiple ways, providing a result where output may be single or double ended. However, the most commonly used in designing a differential amplifier is the double ended, wherein two inputs provide two outputs, called a fully differential amplifier. Its advantage over single ended is simple biasing, high linearity, and high immunity to noise. But it has a large area to cover.

2.5 Procedure:

STEPS FOR THE ANALOG LAB

- Login to **redhat** operating system with the respective login name and password provided in the lab.
- Right click on the screen and select **Open Terminal** to open the command prompt.
- To enter into csh shell type **csh** in the command line.
- To source the cadence tools type **source /cshrc/cad** in the command line.
- To open the tool type **virtuoso &** in the command line.

Creating the Library

- Creating a new library by going to the link **File -> New -> Library**
- Give the library name and click ok.
- Select **attach to an existing technology library** and click **ok**.
- Select **gpd180** and click **ok**.

SCHEMATIC AND SYMBOL CREATION


- In the Library manager select given library
- In Library manager select **File -> New -> Cell view**.
- Give the cell name as csamp.
- Virtuoso Schematic Editor will open.
- Select Create -> Instance, and select the required components (pmos & nmos symbols)
- Select **Create -> pins**, and place the ports (vin, vdd, gnd, vout) on the editor.
- Make the complete connection by using wires by selecting **create -> wire (narrow)**
- After complete of the schematic, save the file by **file -> check & save**


2.6 Observations:

i) COMMON SOURCE AMPLIFIER & COMMON DRAIN AMPLIFIER

COMMON SOURCE AMPLIFIER

COMMON SOURCE SCHEMATIC

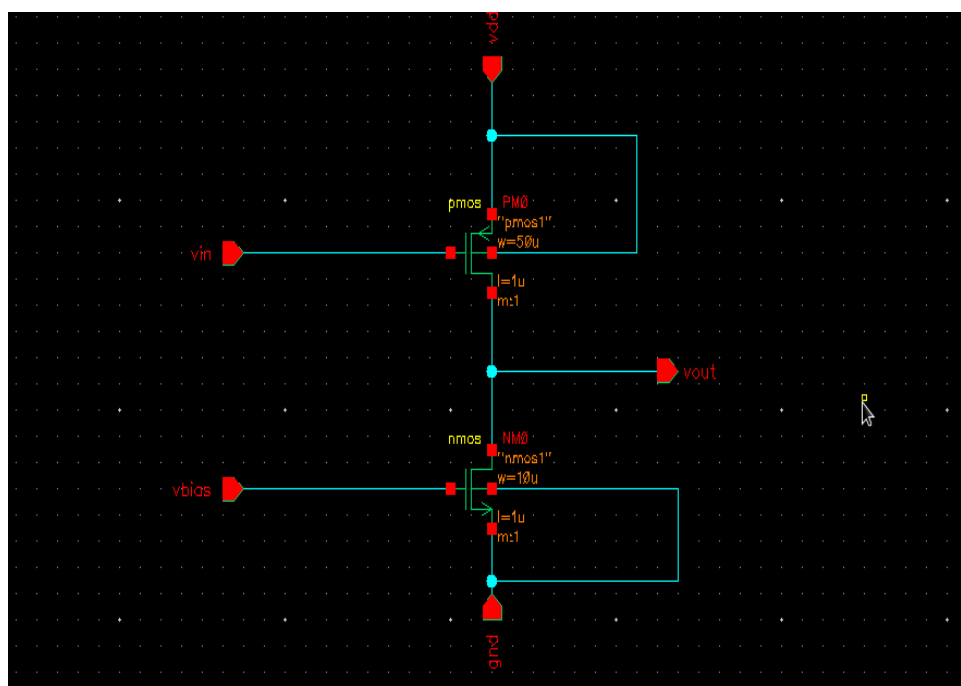

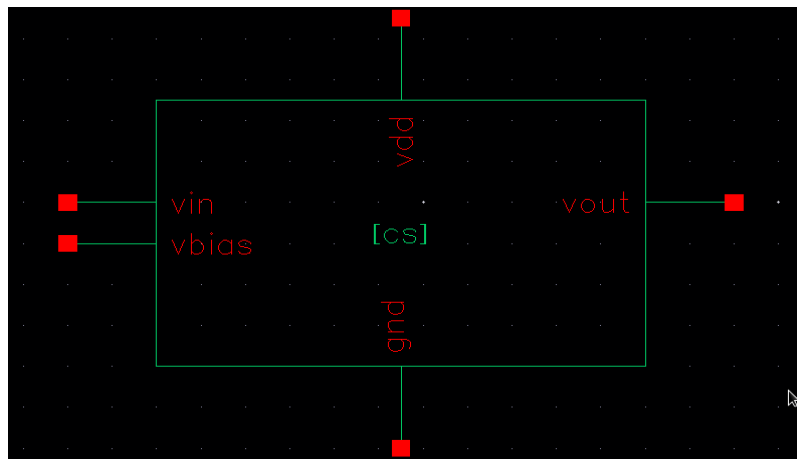COMMON SOURCE SYMBOL

- To create symbol **Create -> Cell View -> From Cell view.**
- Virtuoso symbol editor opens.
- Place the right, left, bottom and top pins.
- Create shape of the cell using option in **Create -> Shapes.**

BUILDING THE TEST DESIGN FOR THE CELL

- In the library manager select given library
- Select **File -> New -> Cell view.**
- Give the cell name as **csamp_test.**
- Virtuoso Schematic editor window will open.
- Select **create -> instance**, and select the design to test.
- To apply inputs, **create -> instance.** In the library select **analoglib** and select appropriate inputs (vpulse, vdc, gnd).


Library name	Cell Name	Properties/Comments
gpd180	pmos	Model Name = pmos1; W= 50u ; L= 1u
gpd180	nmos	Model Name =nmos1; W= 10u ; L= 1u

If the width is 50u or more than that, then divide the mos i.e transistors into parts so for that click on the nmos or pmos properties, and keep

Total Width=50u

Finger Width=25u

Fingers=2

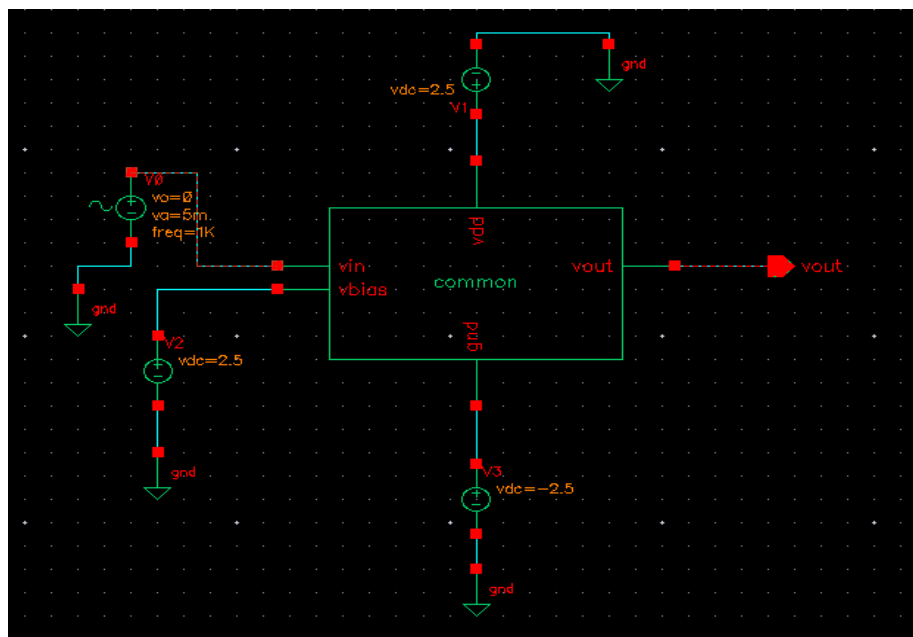COMMON SOURCE SYMBOL TEST**STEPS TO SIMULATE**


- In the Virtuoso Schematic Editor after completing the test circuit design **launch->ADEL**
- Virtuoso Analog Design Environment window opens.
- Go to **Analyses -> choose**, give appropriate inputs for **tran** for transient analyses, **ac** for ac analyses and **dc** for dc analyses.
- Go to **outputs -> to be plotted -> select on schematic** (input and output wires).
- Go to **simulation -> netlist and run**
- When simulation finishes, the Transient, DC plots automatically will be popped up along with log file
- To save the waveform, go to **session** in the ADEL window and in session select **save state**, under it click on **cell view** and then okay.

STEPS FOR CREATING LAYOUT VIEW

- From the **csamp** schematic window menu execute **Launch – Layout XL**. A **Startup Option** form appears.
- Select **Create New** option. This gives a New Cell View Form
- Check the Cellname (**csamp**), Viewname (**layout**).


- Click **OK** from the New Cellview form.
- LSW and a blank layout window appear along with schematic window.

Adding Components to Layout

- Execute **Connectivity – Generate – All from Source** or click the icon  in the layout editor window, **Generate Layout** form appears. Click **OK** which imports the schematic components in to the Layout window automatically.
- Re arrange the components with in PR-Boundary as shown in the next page.
- Press Shift –f in the layout window to display all the levels.
- To rotate a component, Select the component and execute **Edit –Properties**. Now select the degree of rotation from the property edit form.



 - To Move a component, Select the component and execute **Edit -Move** command.



PHYSICAL VERIFICATION

Select **Assura** → **technology** → **Browse** → click on previous directory(..) until we get a **cad** option → double click on **cad** → **foundary** → **analog** → **180nm** → **assura.tech.lib** → **okay**.

Assura DRC**Running a DRC**

- Open the Inverter layout form the CIW or library manger if you have closed that.
- Select **Assura - Run DRC** from layout window.
- The DRC form appears. The Library and Cellname are taken from the current design window, but rule file may be missing. Select the Technology as **gpd180**. This automatically loads the rule file.

Your DRC form should appear like this

- Click **OK** to start DRC.
- A Progress form will appears. You can click on the watch log file to see the log file.
- When DRC finishes, a dialog box appears asking you if you want to view your DRC results, and then click **Yes** to view the results of this run.
- If there any DRC error exists in the design **View Layer Window (VLW)** and **Error Layer Window (ELW)** appears. Also the errors highlight in the design itself.
- Click **View – Summary** in the ELW to find the details of errors.
- You can refer to rule file also for more information, correct all the DRC errors and **Re – run** the DRC.
- If there are no errors in the layout then a dialog box appears with **No DRC errors found** written in it, click on **close** to terminate the DRC run.

ASSURA LVS

In this section we will perform the LVS check that will compare the schematic netlist and the layout netlist.

Running LVS

- Select **Assura – Run LVS** from the layout window.

The Assura Run LVS form appears. It will automatically load both the schematic and layout view of the cell.

- Change the following in the form and click OK.
- The LVS begins and a Progress form appears.
- If the schematic and layout matches completely, you will get the form displaying **Schematic and Layout Match**.

- If the schematic and layout do not match, a form informs that the LVS completed successfully and asks if you want to see the results of this run.
- Click **Yes** in the form.

LVS debug form appears, and you are directed into LVS debug environment.

- In the **LVS debug form** you can find the details of mismatches and you need to correct all those mismatches and **Re – run** the LVS till you will be able to match the schematic with layout.


ASSURA RCX

In this section we will extract the RC values from the layout and perform analog circuit simulation on the designs extracted with RCX.

Before using RCX to extract parasitic devices for simulation, the layout should match with schematic completely to ensure that all parasites will be backannotated to the correct schematic nets.

Running QRC

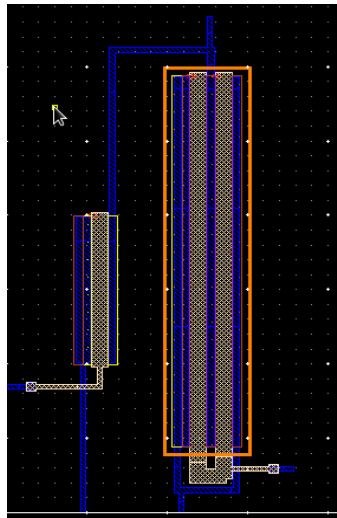- From the layout window execute **Assura – Run QRC**
- In QRC window, under **set up** option select **output as extracted view**,
- Under **Extraction** option, keep **extracted type as RC** and **ref node as gnd! Or vss!**




Steps to obtain Back Annotate Wave

- Select the given library name, and select the schematic test.
- Go to library manager, click on **New** → **cell view** → keep type as **config**
- Below window will appear, select **view as schematic** and select **use template**, under it select **spectre** → **okay**

- In Hierarchy editor window click on **Tree View**, right click on the folder, click on **av_extracted**.
- Click on Open→(schematic test window will be opened)→launch ADEL
- To load the simulated graph ,In ADEL Click on session →load state →cell view →okay
- Once the schematic waveform is loaded, Click on the run symbol in ADEL window to obtain back annotate wave.



 
2.7 Results :

For AC analysis of amplifier, select Sweep Variable as Frequency and Sweep range, start=150 and stop=100M and Sweep type as logarithmic that is 20db.




COMMON DRAIN AMPLIFIER


Library name	Cell Name	Properties/Comments
gpd180	nmos	Model Name = nmos1; W= 50u ; L= 1u
gpd180	nmos	Model Name = nmos1; W= 10u ; L= 1u

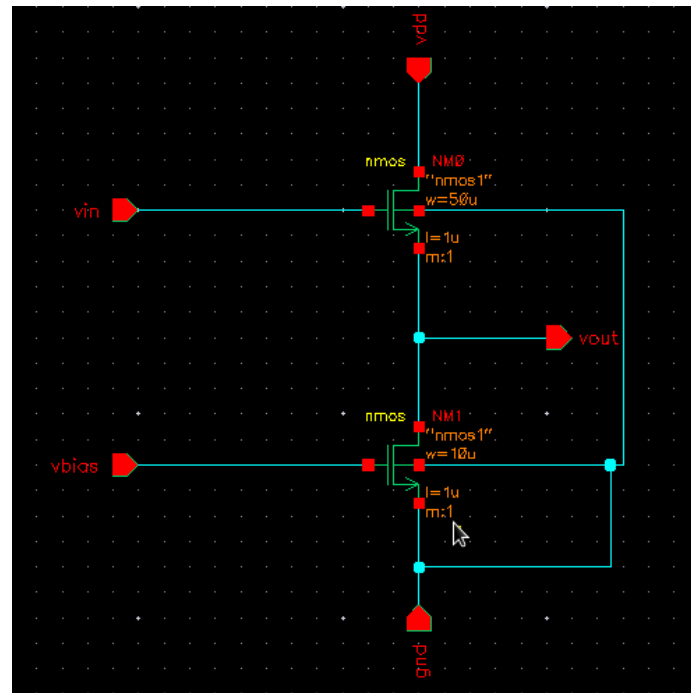 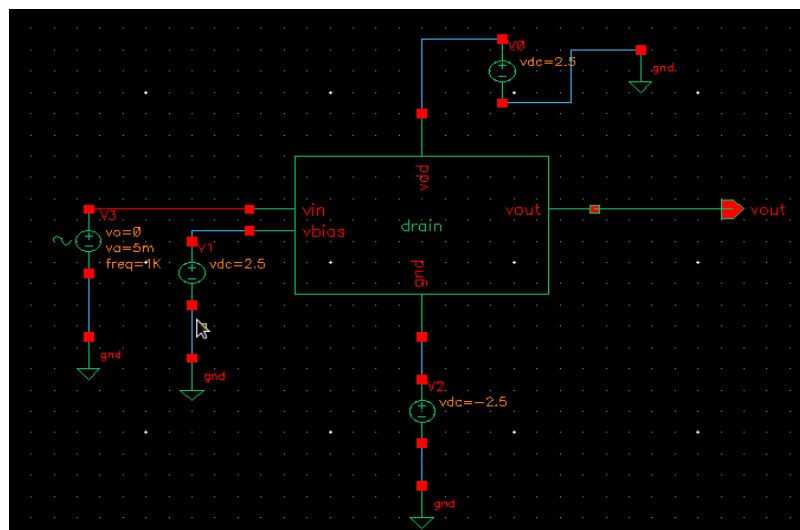COMMON DRAIN SCHEMATIC**COMMON DRAIN SYMBOL****COMMON DRAIN TEST SYMBOL**

COMMON DRAIN WAVEFORM


 




COMMON DRAIN LAYOUT


 


COMMON DRAIN AV EXTRACTED**ii) A SINGLE STAGE DIFFERENTIAL AMPLIFIER**

Library name	Cell Name	Properties/Comments
gpd180	nmos	Model Name = nmos1 (NM0, NM1) ; W= 3u ; L= 1u
gpd180	nmos	Model Name =nmos1 (NM2, NM3) ; W= 4.5u ; L= 1u
gpd180	pmos	Model Name =pmos1 (PM0, PM1); W= 15u ; L= 1u

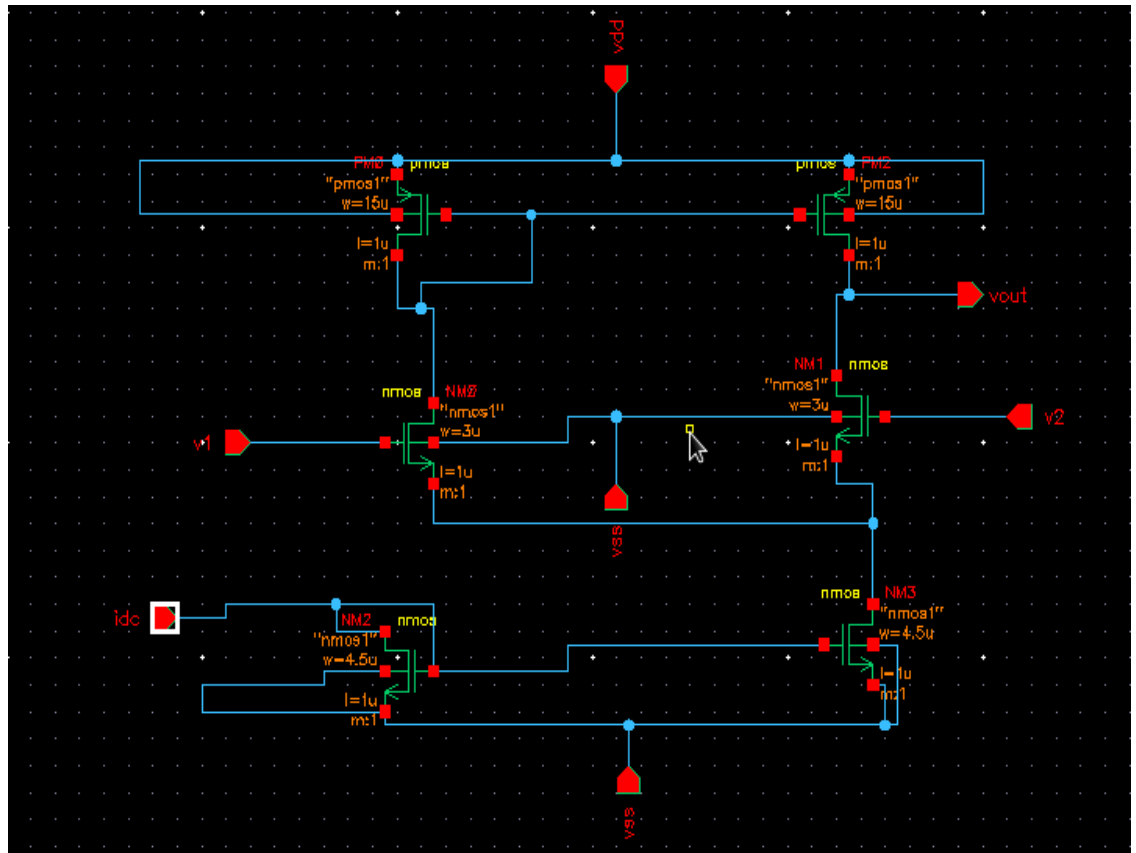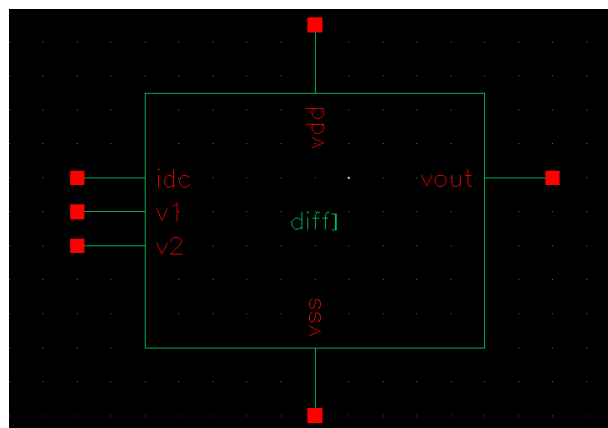DIFFERENTIAL SCHEMATIC**DIFFERENTIAL SYMBOL**

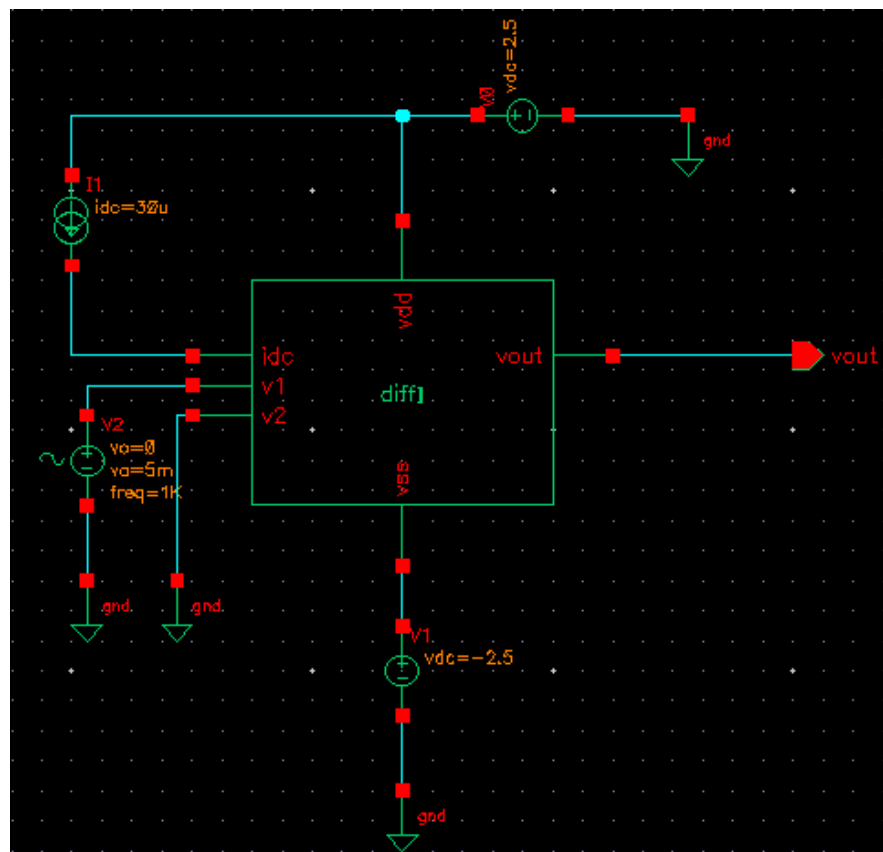 DIFFERENTIAL TEST SYMBOL**DIFFERENTIAL WAVEFORM**

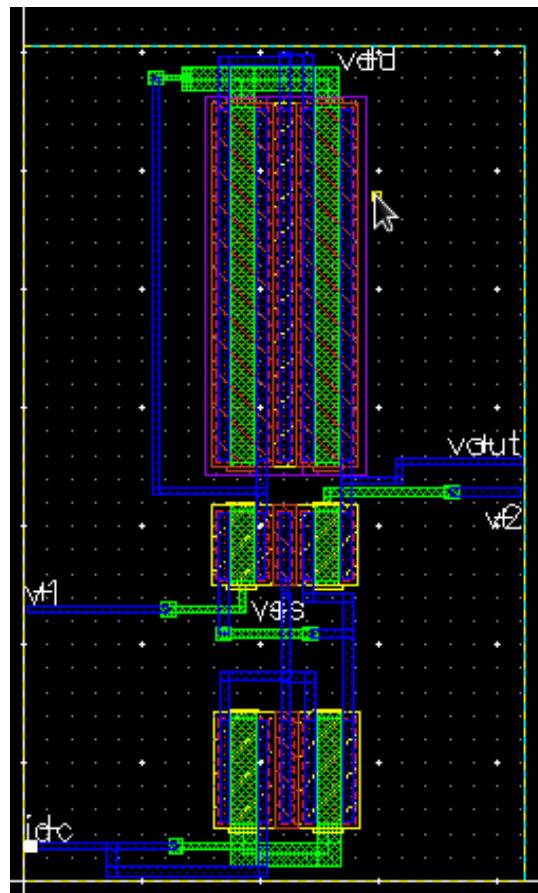 DIFFERENTIAL LAYOUT**DIFFERENTIAL AV EXTRACTED**

2.8 Discussions:

2.9 Pre – Experimentation Questions:

1. What are LVS and DRL tool?
2. What is amplifier.
3. Why W/L ratio is important.
4. What is DC analysis of the circuit.
5. What is AC analysis.

2.10 Post – Experimentation Questions:

1. Explain the functioning of Common Source.
2. Explain the functioning of Common Drain amplifier.
3. Explain the functioning of differential amplifier.
4. Discuss the difference between CS amplifier, CD amplifier and Differential amplifier.
5. What is the necessity of DRC, ERC, QRC.

EXPERIMENT No. 03: Design an op-amp with given specification using given differential amplifier Common source and Common Drain amplifier in library*** and completing the design flow mentioned below:**

- a. Draw the schematic and verify the following
 - i) DC Analysis ii) AC Analysis iii) Transient Analysis
- b. Draw the Layout and verify the DRC, ERC
- c. Check for LVS
- d. Extract RC and back annotate the same and verify the Design.

3.1 Objective	3.6 Observation
3.2 Apparatus Required	3.7 Results
3.3 Pre-Requisite	3.8 Discussions
3.4 Introduction	3.9 Pre-Requisite Question
3.5 Procedure	3.10 Post-Requisite

3.1 Objectives:

Design an op-amp with given specifications and complete design till layout and verify the parameters DRC, ERC, QRC. Extract RC and back annotate for the verification.

3.2 Apparatus Required:

Cadence Tools.

3.3 Pre-Requisite:

Knowledge of Differential amplifier and common source amplifier.
Creating the layout in cadence.

3.4 Introduction:

Op-amps are linear devices which has nearly all the properties required for not only ideal DC amplification but is used extensively for signal conditioning, filtering and for performing mathematical operations such as addition, subtraction, integration, differentiation etc . Generally an Operational Amplifier is a 3-terminal device.

It consists mainly of an Inverting input denoted by a negative sign, ("-") and the other a Non-inverting input denoted by a positive sign ("+") in the symbol for op-amp. Both these inputs are very high impedance. The output signal of an Operational Amplifier is the magnified difference between the two input signals or in other words the amplified

differential input. Generally the input stage of an Operational Amplifier is often a differential amplifier.

An operational amplifier is a DC-coupled differential input voltage amplifier with a rather high gain. In most general purpose op-amps there is a single ended output. Usually an op-amp produces an output voltage a million times larger than the voltage difference across its two input terminals.

3.5 Procedure:

STEPS FOR THE ANALOG LAB

- Login to **redhat** operating system with the respective login name and password provided in the lab.
- Right click on the screen and select **Open Terminal** to open the command prompt.
- To enter into csh shell type **csh** in the command line.
- To source the cadence tools type **source /cshrc/cad** in the command line.
- To open the tool type **virtuoso &** in the command line.

Creating the Library


- Creating a new library by going to the link **File -> New -> Library**
- Give the library name and click ok.
- Select **attach to an existing technology library** and click **ok**.
- Select **gpd180** and click **ok**.

SCHEMATIC AND SYMBOL CREATION


- In the Library manager select given library
- In Library manager select **File -> New -> Cell view**.
- Give the cell name as opamp
- Virtuoso Schematic Editor will open.
- Select Create -> Instance, and select the required components (pmos & nmos symbols)
- Select **Create -> pins**, and place the ports (vin, vdd, gnd, vout) on the editor.
- Make the complete connection by using wires by selecting **create -> wire (narrow)**
- After complete of the schematic, save the file by **file -> check & save**

3.6 Observations:

OPAMP SCHEMATIC

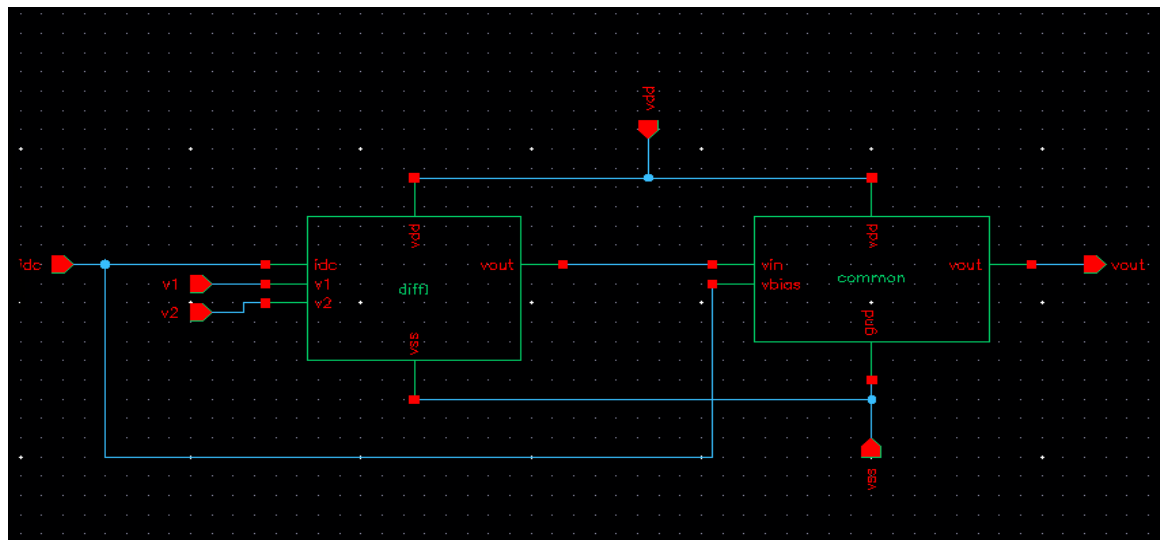

OPAMP SYMBOL

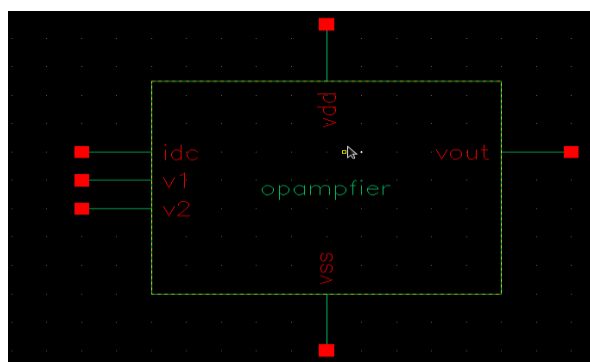

- To create symbol **Create -> Cell View -> From Cell view.**
- Virtuoso symbol editor opens.
- Place the right, left, bottom and top pins.
- Create shape of the cell using option in **Create -> Shapes.**


BUILDING THE TEST DESIGN FOR THE CELL

- In the library manager select given library
- Select **File -> New -> Cell view.**
- Give the cell name as **opamp_test.**
- Virtuoso Schematic editor window will open.

- Select **create -> instance**, and select the design to test.
- To apply inputs, **create -> instance**. In the library select **analoglib** and select appropriate inputs (vpulse, vdc, gnd).

Library name	Cell Name	Properties/Comments
myDesignLib	Diff_amplifier	Symbol
myDesignLib	cs_amplifier	Symbol

OPAMP TEST SYMBOL

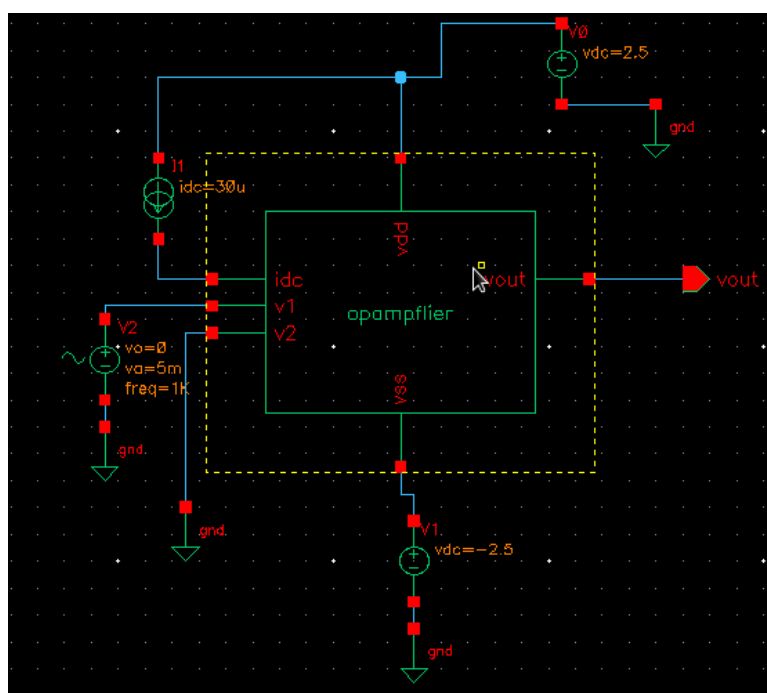

STEPS TO SIMULATE


- In the Virtuoso Schematic Editor after completing the test circuit design **launch->ADEL**
- Virtuoso Analog Design Environment window opens.
- Go to **Analyses -> choose**, give appropriate inputs for **tran** for transient analyses and **dc** for dc analyses.
- Go to **outputs -> to be plotted -> select on schematic** (input and output wires).
- Go to **simulation -> netlist and run**

- When simulation finishes, the Transient, DC plots automatically will be popped up along with log file.
- To save the waveform, go to **session** in the ADEL window and in session select **save state**, under it click on **cell view** and then okay.

STEPS FOR CREATING LAYOUT VIEW


- From the **Inverter** schematic window menu execute **Launch – Layout XL**. A **Startup Option** form appears.
- Select **Create New** option. This gives a New Cell View Form
- Check the Cellname (**Inverter**), Viewname (**layout**).
- Click **OK** from the New Cellview form.
- LSW and a blank layout window appear along with schematic window.

Adding Components to Layout

- Execute **Connectivity – Generate – All from Source** or click the icon  in the layout editor window, **Generate Layout** form appears. Click **OK** which imports the schematic components in to the Layout window automatically.
- Re arrange the components with in PR-Boundary as shown in the next page.
- Press Shift –f in the layout window to display all the levels.
- To rotate a component, Select the component and execute **Edit –Properties**. Now select the degree of rotation from the property edit form.



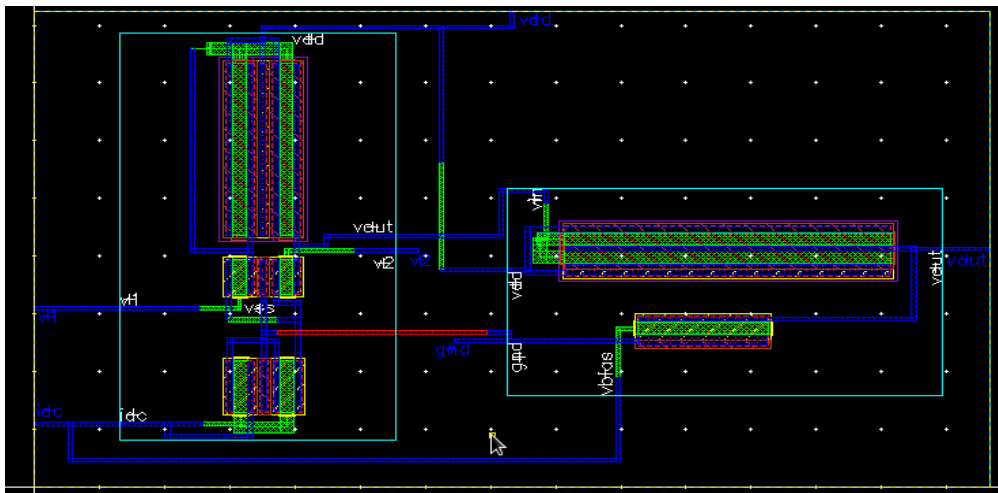- To Move a component, Select the component and execute **Edit -Move** command.



PHYSICAL VERIFICATION

Select **Assura** → **technology** → **Browse** → click on previous directory(..) until we get a **cad** option → double click on **cad** → **foundary** → **analog** → **180nm** → **assura.tech.lib** → **okay**.

Assura DRC**Running a DRC**

- Open the Inverter layout form the CIW or library manger if you have closed that.
- Select **Assura - Run DRC** from layout window.
- The DRC form appears. The Library and Cellname are taken from the current design window, but rule file may be missing. Select the Technology as **gpd180**. This automatically loads the rule file.

Your DRC form should appear like this

- Click **OK** to start DRC.
- A Progress form will appears. You can click on the watch log file to see the log file.
- When DRC finishes, a dialog box appears asking you if you want to view your DRC results, and then click **Yes** to view the results of this run.
- If there any DRC error exists in the design **View Layer Window (VLW)** and **Error Layer Window (ELW)** appears. Also the errors highlight in the design itself.
- Click **View – Summary** in the ELW to find the details of errors.
- You can refer to rule file also for more information, correct all the DRC errors and **Re – run** the DRC.
- If there are no errors in the layout then a dialog box appears with **No DRC errors found** written in it, click on **close** to terminate the DRC run.

ASSURA LVS

In this section we will perform the LVS check that will compare the schematic netlist and the layout netlist.

Running LVS

- Select **Assura – Run LVS** from the layout window.

The Assura Run LVS form appears. It will automatically load both the schematic and layout view of the cell.

- Change the following in the form and click OK.

- The LVS begins and a Progress form appears.
- If the schematic and layout matches completely, you will get the form displaying **Schematic and Layout Match**.
- If the schematic and layout do not matches, a form informs that the LVS completed successfully and asks if you want to see the results of this run.
- Click **Yes** in the form.

LVS debug form appears, and you are directed into LVS debug environment.

- In the **LVS debug form** you can find the details of mismatches and you need to correct all those mismatches and **Re – run** the LVS till you will be able to match the schematic with layout.


ASSURA RCX

In this section we will extract the RC values from the layout and perform analog circuit simulation on the designs extracted with RCX.

Before using RCX to extract parasitic devices for simulation, the layout should match with schematic completely to ensure that all parasites will be backannotated to the correct schematic nets.


Running QRC

- From the layout window execute **Assura – Run QRC**
- In QRC window, under **set up** option select **output as extracted view**,
- Under **Extraction** option, keep **extracted type as RC** and **ref node as gnd! Or vss!**

 OPAMP AV EXTRACTED**Steps to obtain Back Annotate Wave**

- Select the given library name, and select the schematic test.
- Go to library manager, click on **New** → **cell view** → keep type as **config**
- Below window will appear, **select view as schematic** and **select use template**, under it **select spectre** → **okay**
- In Hierarchy editor window click on **Tree View**, right click on the folder, click on **av_extracted**.
- Click on **Open** → (schematic test window will be opened) → launch ADEL
- To load the simulated graph, In ADEL Click on **session** → **load state** → **cell view** → **okay**
- Once the schematic waveform is loaded, Click on the run symbol in ADEL window to obtain back annotate wave.

3.7 Results :

 

3.8 Discussions:

3.9 Pre – Experimentation Questions:

1. Define op-amp
2. Discuss the application of op-amp.
3. Explain different parameters of op-amp.
4. Explain the working of differential amplifier.
5. Explain the working of common source amplifier.

3.10 Post – Experimentation Questions:

1. Discuss the application of op-amp.
2. Explain the characteristics of the op-amp.
3. How inverting and non-inverting op-amp can be designed.
4. Define CMRR for an op-amp
5. Discuss the waveforms generated.

EXPERIMENT No. 04: Design a 4 bit R-2R based DAC for the given specification and completing the design flow mentioned using given op-amp in the library*.**

a. Draw the schematic and verify the following

i) DC Analysis

ii) AC Analysis

iii) Transient Analysis

b. Draw the Layout and verify the DRC, ERC

4.1 Objective	4.6 Observation
4.2 Apparatus Required	4.7 Results
4.3 Pre-Requisite	4.8 Discussions
4.4 Introduction	4.9 Pre-Requisite Question
4.5 Procedure	4.10 Post-Requisite

4.1 Objectives:

Design a 4 bit R-2R DAC with given specifications and complete design till layout and verify the parameters DRC,ERC.

4.2 Apparatus Required:

Cadence Tools.

4.3 Pre-Requisite:

Knowledge of Differential amplifier, common source amplifier and op-amp. Creating the layout in cadence.

4.4 Introduction

R-2R Ladder, which uses fewer unique resistor values thus does not require precision resistors. A disadvantage of the former DAC design was its requirement of several different precise input resistor values: one unique value per binary input bit. Its advantage comparing to the binary weighted is it only has two values of resistors, thus the actual values used is relatively less important if it is extremely large values. The staircase voltage result is more likely to be monotonic as the effect of the MSB resistor is not many times greater than that for LSB resistor.

4.5 Procedure:

STEPS FOR THE ANALOG LAB

- Login to **redhat** operating system with the respective login name and password provided in the lab.
- Right click on the screen and select **Open Terminal** to open the command prompt.
- To enter into csh shell type **csh** in the command line.
- To source the cadence tools type **source /cshrc/cad** in the command line.
- To open the tool type **virtuoso &** in the command line.

Creating the Library


- Creating a new library by going to the link **File -> New -> Library**
- Give the library name and click ok.
- Select **attach to an existing technology library** and click **ok**.
- Select **gpd180** and click **ok**.

SCHEMATIC AND SYMBOL CREATION

- In the Library manager select given library
- In Library manager select **File -> New -> Cell view**.
- Give the cell name as R-2R.
- Virtuoso Schematic Editor will open.
- Select Create -> Instance, and select the required components (pmos & nmos symbols)
- Select **Create -> pins**, and place the ports (vin, vdd, gnd, vout) on the editor.
- Make the complete connection by using wires by selecting **create -> wire (narrow)**
- After complete of the schematic, save the file by **file -> check & save**


4.6 Observations:

R-2R DAC SCHEMATIC

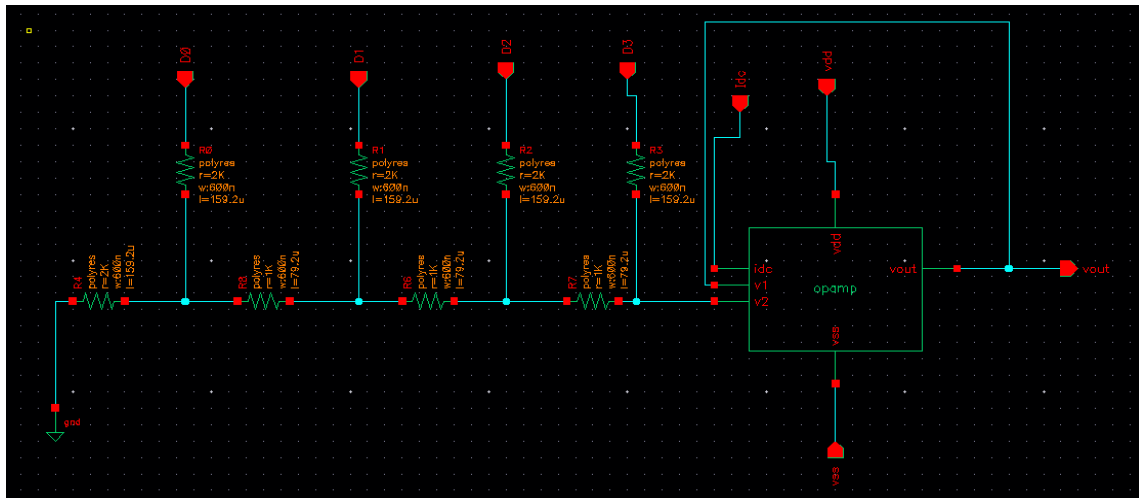

Library name	Cell Name	Properties/Comments
gpdk180	Polyres	R = 2k
gpdk180	Polyres	R = 1k
MyDesignLib	op-amp	Symbol
AnalogLib	Idc, gnd	idc = 30u

Pin Names	Direction
D0 D1 D2 D3	Input
Vout	Output
vdd, vss	Input

 R-2R DAC SYMBOL


- To create symbol **Create -> Cell View -> From Cell view.**
- Virtuoso symbol editor opens.
- Place the right, left, bottom and top pins.

Create shape of the cell using option in **Create -> Shapes**

BUILDING THE TEST DESIGN FOR THE CELL

- In the library manager select given library
- Select **File -> New -> Cell view.**
- Give the cell name as **R-2R_test.**
- Virtuoso Schematic editor window will open.
- Select **create -> instance**, and select the design to test.
- To apply inputs, **create -> instance**. In the library select **analoglib** and select appropriate inputs (vpulse, vdc, gnd).

Library name	Cellview name	Properties/Comments
myDesignLib	R-2R-DAC	Symbol
analogLib	Vpulse	For V0: v1= 0 v2 = 2 Ton = 5n T = 10n For V1: v1= 0 v2 = 2 Ton = 10n T = 20n For V2: v1= 0 v2 = 2 Ton = 20n T = 40n For V3: v1= 0 v2 = 2 Ton = 40n T = 80n
analogLib	vdc, gnd	vdd = 2.5 vss = -2.5
analogLib	Idc	Idc=30ua

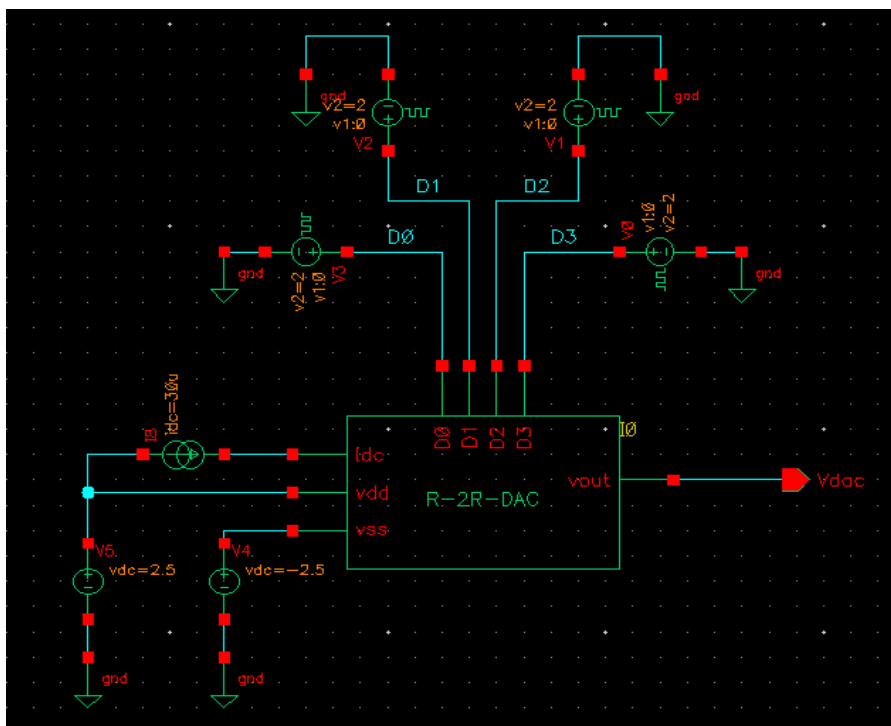R-2R TEST SYMBOL**STEPS TO SIMULATE**


- In the Virtuoso Schematic Editor after completing the test circuit design **launch->ADEL**
- Virtuoso Analog Design Environment window opens.
- Go to **Analyses -> choose**, give appropriate inputs for **tran** for transient analyses and **dc** for dc analyses.
- Go to **outputs -> to be plotted -> select on schematic** (input and output wires).
- Go to **simulation -> netlist and run**
- When simulation finishes, the Transient, DC plots automatically will be popped up along with log file.
- To save the waveform, go to **session** in the ADEL window and in session select **save state**, under it click on **cell view** and then okay.


STEPS FOR CREATING LAYOUT VIEW

- From the **Inverter** schematic window menu execute **Launch – Layout XL**. A **Startup Option** form appears.
- Select **Create New** option. This gives a New Cell View Form
- Check the Cellname (**Inverter**), Viewname (**layout**).

- Click **OK** from the New Cellview form.
- LSW and a blank layout window appear along with schematic window.

Adding Components to Layout

- Execute **Connectivity – Generate – All from Source** or click the icon  in the layout editor window, **Generate Layout** form appears. Click **OK** which imports the schematic components in to the Layout window automatically.
- Re arrange the components with in PR-Boundary as shown in the next page.
- Press Shift –f in the layout window to display all the levels.
- To rotate a component, Select the component and execute **Edit –Properties**. Now select the degree of rotation from the property edit form.

 

PHYSICAL VERIFICATION

Select **Assura** → **technology** → **Browse** → click on previous directory(..) until we get a **cad** option → double click on **cad** → **foundary** → **analog** → **180nm** → **assura.tech.lib** → **okay**.

Assura DRC

Running a DRC

- Open the Inverter layout form the CIW or library manger if you have closed that.
- Select **Assura - Run DRC** from layout window.
- The DRC form appears. The Library and Cellname are taken from the current design window, but rule file may be missing. Select the Technology as **gpd180**. This automatically loads the rule file.

Your DRC form should appear like this

- Click **OK** to start DRC.

- A Progress form will appear. You can click on the watch log file to see the log file.
- When DRC finishes, a dialog box appears asking you if you want to view your DRC results, and then click **Yes** to view the results of this run.
- If there any DRC error exists in the design **View Layer Window (VLW)** and **Error Layer Window (ELW)** appears. Also the errors highlight in the design itself.
- Click **View – Summary** in the ELW to find the details of errors.
- You can refer to rule file also for more information, correct all the DRC errors and **Re – run** the DRC.
- If there are no errors in the layout then a dialog box appears with **No DRC errors found** written in it, click on **close** to terminate the DRC run.

ASSURA LVS

In this section we will perform the LVS check that will compare the schematic netlist and the layout netlist.

Running LVS

- Select **Assura – Run LVS** from the layout window.

The Assura Run LVS form appears. It will automatically load both the schematic and layout view of the cell.

- Change the following in the form and click OK.
- The LVS begins and a Progress form appears.
- If the schematic and layout matches completely, you will get the form displaying **Schematic and Layout Match**.
- If the schematic and layout do not match, a form informs that the LVS completed successfully and asks if you want to see the results of this run.
- Click **Yes** in the form.

LVS debug form appears, and you are directed into LVS debug environment.


- In the **LVS debug form** you can find the details of mismatches and you need to correct all those mismatches and **Re – run** the LVS till you will be able to match the schematic with layout.

ASSURA RCX

- In this section we will extract the RC values from the layout and perform analog circuit simulation on the designs extracted with RCX.

- Before using RCX to extract parasitic devices for simulation, the layout should match with schematic completely to ensure that all parasites will be backannotated to the correct schematic nets.

4.7 Results :

 

4.8 Discussions

4.9 Pre-Requisite Question


1. What are the design rules and explain them
2. Discuss the functioning of op-amp.
3. What is R-2R based DAC.
4. What is gpd90.
5. What are the different technologies used for designing in Cadence.

4.10 Post-Requisite Question

1. Explain the working R-2R DAC.
2. Discuss the circuit design of R-2R based DAC.
3. Discuss the waveforms generated for the same.
4. Explain sampling and hold method.
5. Explain the technology gpd180.

EXPERIMENT No. 05: For the SAR based ADC mentioned in the figure below draw the mixed signal schematic and verify the functionality by completing ASIC Design FLOW.

[Specifications to GDS-II]

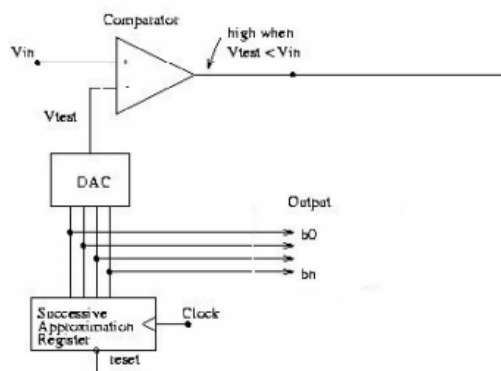

5.1 Objective

5.2 Apparatus Required

5.3 Pre-Requisite

5.4 Introduction

5.5 Project

5.6 Results

5.7 Discussions

5.8 Pre-Requisite Question

5.9 Post-Requisite

5.1 Objectives:

Design an op-amp with given specifications and complete design till layout and verify the parameters DRC, ERC, QRC. Extract RC and back annotate for the verification.

5.2 Apparatus Required:

Cadence Tools.

5.3 Pre-Requisite:

Knowledge of Differential amplifier and common source amplifier, op-amp. Creating the layout in cadence.

5.4 Introduction:

A SAR ADC uses a series of comparisons to determine each bit of the converted result. Therefore, a SAR ADC needs at least $n+1$ clock cycles to convert an analog input to the ADC to a result, where n is the number of bits of the ADC. The analog input is tracked by the SAR ADC, then sampled and held during the conversion.

5.5 Project:

****THIS EXPERIMENT WILL BE GIVEN AS MINI-PROJECT****

5.6 Discussions:

5.7 Results

5.8 Pre-Requisite Question

1. Discuss the functioning of CS amplifier.
2. What is differential amplifier and explain the functioning.
3. Explain the functioning of op-amp.
4. Explain the characteristics of op-amp.
5. Draw the waveform generated by op-amp and analyze.

5.9 Post-Requisite Question

1. Explain sampling and hold.
2. Discuss the working of ADC
3. What is the application of SAR.
4. Explain the waveform generated by SAR.
5. What is the function of ADC.